

EECS 411 - Microwave Circuits

①

Transmission Line Theory.

Lossless Transmission Lines.

> Telegrapher's Equations

$$\frac{\partial^2 V}{\partial z^2} = LC \frac{\partial^2 V}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial z^2} = LC \frac{\partial^2 i}{\partial t^2}$$

> general solution is of the form $V(z, t) = F(z \pm ut)$

$$i(z, t) = F(z \pm ut)$$

> where u is the velocity of propagation of the signal. Substituting them into the Telegrapher's Equations gives $\boxed{u = \frac{1}{\sqrt{LC}}}$

$$\begin{aligned} \text{Therefore, } V &= V^+(z - \frac{1}{\sqrt{LC}}t) + V^-(z + \frac{1}{\sqrt{LC}}t) \\ i &= i^+(z - \frac{1}{\sqrt{LC}}t) + i^-(z + \frac{1}{\sqrt{LC}}t) \end{aligned} \quad \left. \vphantom{\begin{aligned} V &= V^+(z - \frac{1}{\sqrt{LC}}t) + V^-(z + \frac{1}{\sqrt{LC}}t) \\ i &= i^+(z - \frac{1}{\sqrt{LC}}t) + i^-(z + \frac{1}{\sqrt{LC}}t) \end{aligned}} \right\} \begin{array}{l} \text{General} \\ \text{solutions of 2} \\ \text{waves.} \end{array}$$

> Apply $\frac{\partial V}{\partial z} = -L \frac{\partial i}{\partial t} \Rightarrow V^+ = \sqrt{\frac{L}{C}} i^+$ and $V^- = -\sqrt{\frac{L}{C}} i^-$

Therefore, we define $\boxed{Z_0 = \sqrt{\frac{L}{C}}}$ $V^+ = Z_0 i^+$; $V^- = -Z_0 i^-$

> Using phasor notation and assuming sinusoidal solutions.

$$\left. \begin{aligned} \frac{d^2 V}{dz^2} &= -\omega^2 LC V \\ \frac{d^2 I}{dz^2} &= -\omega^2 LC I \end{aligned} \right\} \begin{array}{l} \text{Telegrapher's} \\ \text{Equations.} \end{array}$$

Let $\boxed{\beta = \omega \sqrt{LC}}$
phase constant.

Relative permittivity $\epsilon_r = \left(\frac{c}{u_g} \right)^2$

The general solutions now become,

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} = V^+(z) + V^-(z)$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} = I^+(z) + I^-(z)$$

Converting back to time domain (x with $e^{j\omega t}$ & take Re part)

$$V(z, t) = V_0^+ \cos(\omega t - \beta z) + V_0^- \cos(\omega t + \beta z)$$

$$I(z, t) = I_0^+ \cos(\omega t - \beta z) + I_0^- \cos(\omega t + \beta z)$$

$$\boxed{u = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}} \quad \text{Phase velocity.}$$

$$\boxed{\beta = \frac{2\pi}{\lambda} = \omega \sqrt{LC}} \quad \text{phase constant}$$

$$V^+ = (V + i Z_0 I) / 2$$


$$I^+ = (I + Y_0 V) / 2 \quad Y_0 = \frac{1}{Z_0}$$

$$V^- = (V - i Z_0 I) / 2$$

$$I^- = (I - Y_0 V) / 2$$

Reflection Coefficient
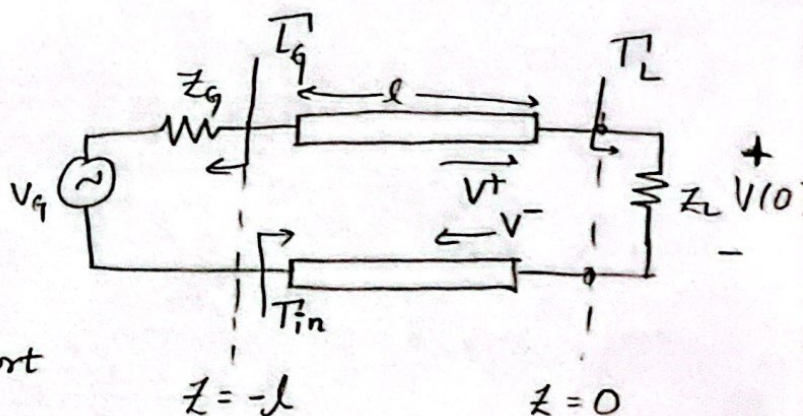
$$\Gamma = \frac{V^-}{V^+} = \frac{Z(z) - Z_0}{Z(z) + Z_0}$$



$$\boxed{\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}}$$


$$\Gamma_L = -1 \Rightarrow \text{Short}$$

$$\Gamma_L = 1 \Rightarrow \text{open.}$$

$$\Gamma_L = 0 \Rightarrow \text{matched.}$$

Transmission Coefficient
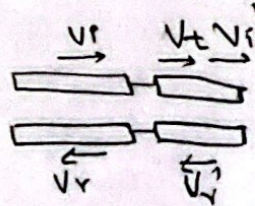
$$\tau_L = \frac{V(0)}{V^+(0)} = \frac{V^+(0) + V^-(0)}{V^+(0)} = 1 + \Gamma_L = \frac{2 Z_L}{Z_L + Z_0}$$



$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}$$

$$\Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}$$

$$\tau_L = \frac{V_t}{V_i} = \frac{V_i + V_r}{V_i} = \frac{V_i' + V_r'}{V_i}$$

Power

Average power $\langle P \rangle = \frac{1}{T} \int_0^T v(t) i(t) dt$

In phasor $\langle P \rangle = \frac{1}{2} \operatorname{Re}[V I^*]$


$$P_i = \frac{1}{2} \frac{|V|^2}{|Z_0|}$$

$$P_r = \frac{1}{2} \frac{|V|^2}{|Z_0|}$$

$$= \frac{1}{2} \frac{|V|^2}{|Z_0|} \cdot |T|^2$$

$$\boxed{\begin{aligned} \frac{P_r}{P_i} &= |T|^2 \\ \frac{P_t}{P_i} &= 1 - |T|^2 \end{aligned}}$$

General form of T

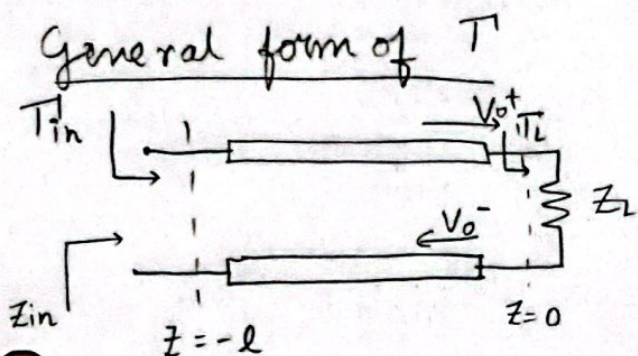

$$\boxed{T_{in} = T_L e^{-2j\beta l}}$$

$\Rightarrow$ only phase change along lossless line

$$Z_{in} = Z_0 \cdot \frac{1 + T_L e^{-2j\beta l}}{1 - T_L e^{-2j\beta l}} = Z_0 \frac{1 + T_{in}}{1 - T_{in}}$$

$$\boxed{Z_{in} = Z_0 \cdot \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}}$$



βl = electrical length in degrees.

$$\theta = \beta l = 2\pi \frac{l}{\lambda}$$

> βl is a measure of how many wavelengths can fit inside the line. More wavelengths can fit $\Rightarrow$ high βl .

> T and Z are repeated every $\lambda/2$ along the line.
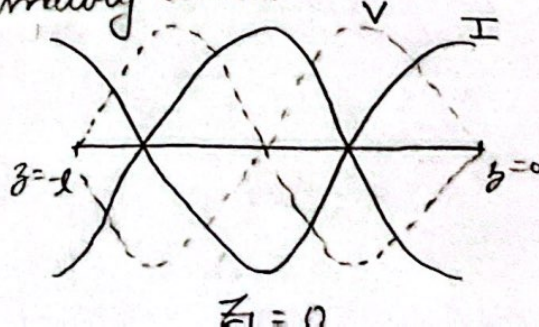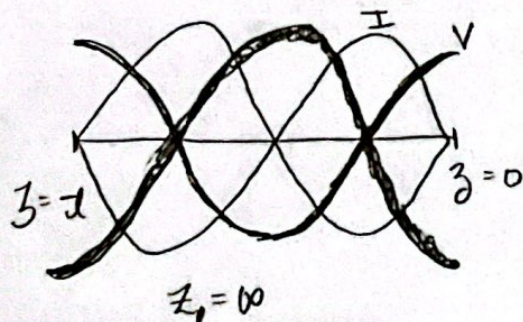
> $Z_L = \infty, 0 \Rightarrow$ standing waves on the line & V, I are 90° out of phase due to boundary condition.



Voltage Standing Wave Ratio. (VSWR)

$$\boxed{VSWR = \frac{V_{max}}{V_{min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}} \quad ; \quad |\Gamma| = \frac{VSWR - 1}{VSWR + 1}$$

$VSWR = \infty \Rightarrow$ pure standing wave $\Rightarrow Z_L = 0, \infty$


$VSWR = 1 \Rightarrow$ only travelling wave $\Rightarrow Z_L = Z_0$.

Short circuited line.

$$\boxed{Z_{short} = j Z_0 \tan \beta l}$$

$l < \lambda/4 \Rightarrow$ inductor. with inductance
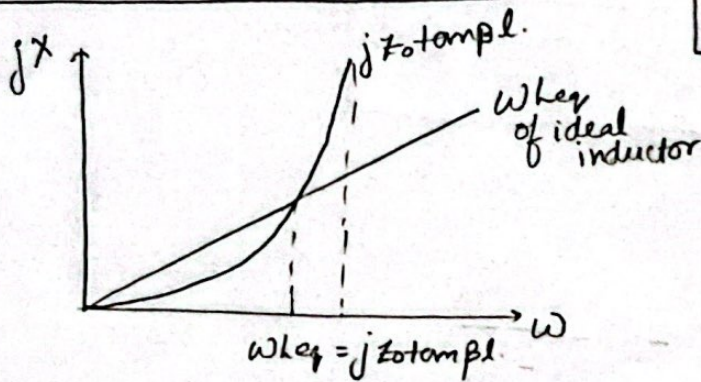
$$\boxed{L_{eq} = \frac{Z_0}{\omega} \tan \beta l}$$



Open circuited line.

$$\boxed{Z_{open} = -j Z_0 \cot \beta l}$$

$l < \lambda/4 \Rightarrow$ Capacitor with capacitance

$$\boxed{C_{eq} = \frac{Y_0}{\omega} \tan \beta l}$$

Quarter wave Transformer.

$$\boxed{Z_{in} = \frac{Z_0^2}{R_L}}$$

$\Rightarrow$ To deliver maximum power

$$Z_0 = \sqrt{R_G R_L}$$

↓
must be real.

Lossy Transmission Lines.

(2)

Let $Z = R + j\omega L$ $Y = G + j\omega C$, $\gamma^2 = ZY$

$\frac{d^2 V(z)}{dz^2} = \gamma^2 V(z)$; $\frac{d^2 I(z)}{dz^2} = \gamma^2 I(z)$ } Freq. domain telegraphers equations with sinusoidal excitation

$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta$

γ : complex prop. constant
 α : attenuation constant
 β : phase constant

α : Nepers/meter.
 β : Radians/meter.

Solutions to Telegraphers

$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$
 $I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$

$\boxed{dB/m = 8.686 \text{ Nepers/m}}$

$\boxed{Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}}}$

Time domain Solutions


$v(z,t) = V_0^+ e^{-\alpha z} \cos(\omega t - \beta z) + V_0^- e^{-\alpha z} \cos(\omega t + \beta z)$
 $i(z,t) = \frac{1}{Z_0} [V_0^+ e^{-\alpha z} \cos(\omega t - \beta z) - V_0^- e^{-\alpha z} \cos(\omega t + \beta z)]$

Phase velocity: $\boxed{u_p = \frac{\omega}{\beta}}$ and $\boxed{\beta = \frac{2\pi}{\lambda} = \frac{\omega}{u_p}}$

Group velocity: $\boxed{u_g = \frac{d\omega}{d\beta}}$

Velocity of propagation is now a fn of f.
 $\Rightarrow$ Dispersion.

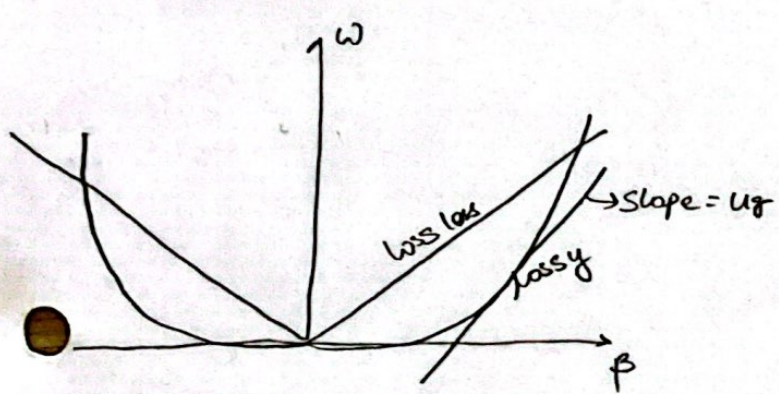Lossless line: $u_g = \frac{d\omega}{d\beta} = \frac{d\omega}{d\omega \sqrt{LC}} = \frac{1}{\sqrt{LC}} = u_p$



> u_p can be greater than u_g
 $\Rightarrow$

> Attenuation after length l
 $\Rightarrow \alpha l$ in Nepers

$\boxed{dB_{loss} = 8.686 \times \alpha l}$

low loss approximation

$$\text{If } R \ll \omega L \text{ and } G \ll \omega C$$

$$\beta \approx \omega \sqrt{LC}, \quad \alpha = \frac{1}{2} \left(\frac{R}{Z_0} + G Z_0 \right), \quad \gamma = \alpha + j\beta$$

$$Z_0 \approx \sqrt{\frac{L}{C}}$$

Integrated Circuit Tlines

$$\text{If } G \approx 0 \text{ and } R \gg \omega L$$

$$\text{Note } \sqrt{j} = \frac{1+j}{\sqrt{2}}$$

$$\alpha = \frac{1}{\sqrt{2}} \sqrt{\omega R C}, \quad \beta = \frac{1}{\sqrt{2}} \sqrt{\omega R C}, \quad \gamma = \alpha + j\beta$$

$$Z_0 = \frac{1-j}{\sqrt{2}} \sqrt{\frac{R}{\omega C}}$$

$$U_p = \sqrt{\frac{2\omega}{RC}}, \quad U_g = 2 \sqrt{\frac{2\omega}{RC}} \Rightarrow U_g \neq U_p \Rightarrow \text{dispersion.}$$

Distortionless lossy Tline.

$$\text{If } \frac{R}{L} = \frac{G}{C}$$

$$\alpha = R \sqrt{\frac{C}{L}}, \quad \beta = \omega \sqrt{LC}, \quad \gamma = \alpha + j\beta$$

$$U_p = U_g = \frac{1}{\sqrt{LC}}$$

Terminated lossy Tline.

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$

$$T_{in} = T_L e^{-2\alpha l} e^{-j\beta l}$$

The Smith Chart

$$Z_{in} = Z_0 \cdot \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}}$$


$$\sigma + jx = \frac{1 + \Gamma_L e^{-2j\beta l}}{1 - \Gamma_L e^{-2j\beta l}}$$

where $\Gamma_{in} = \Gamma_L e^{-2j\beta l} = u + jv$


$$\Rightarrow \bar{Z}_{in} = \frac{1 + u + jv}{1 - (u + jv)} = \sigma + jx \Rightarrow \begin{cases} (u - \frac{r}{1+r})^2 + v^2 = \frac{1}{(1+r)^2} \\ (u-1)^2 + (v - \frac{1}{x})^2 = \frac{1}{x^2} \end{cases}$$

Constant $r \Rightarrow$ Circles centred at $(\frac{r}{1+r}, 0)$, radius $\frac{1}{1+r}$

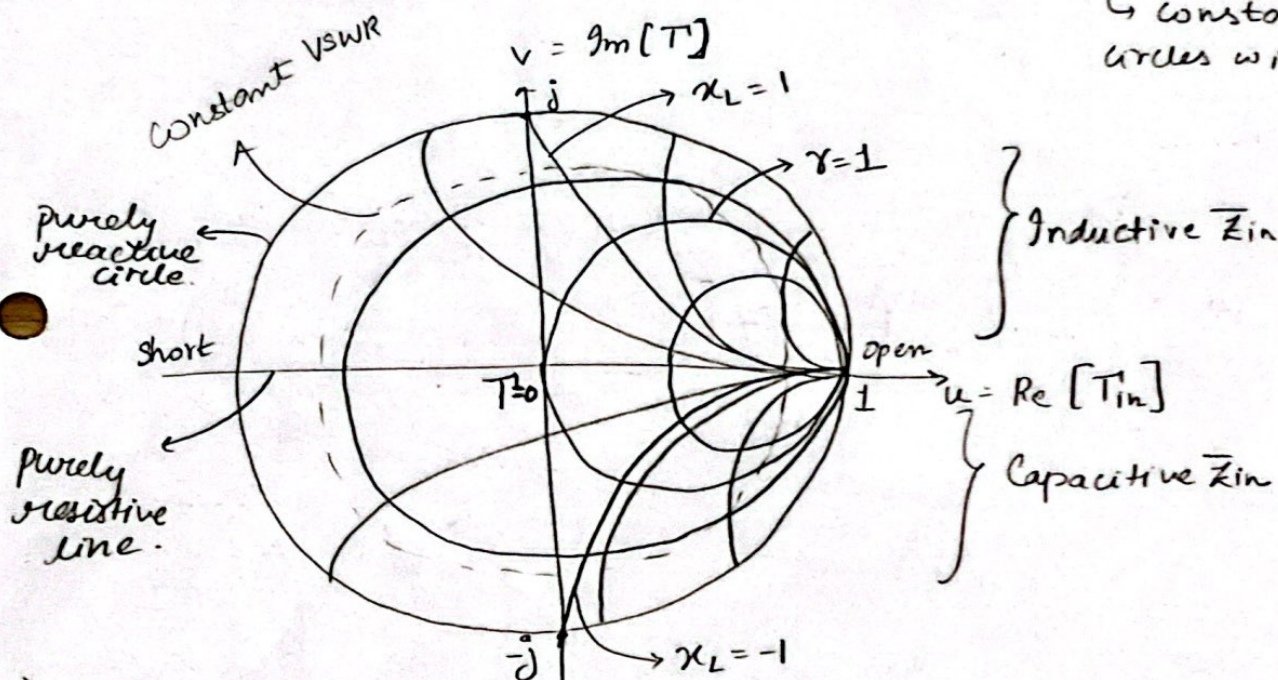Constant $x \Rightarrow$ Circles with $c = (1, \frac{1}{x})$
 $r = \frac{1}{x}$


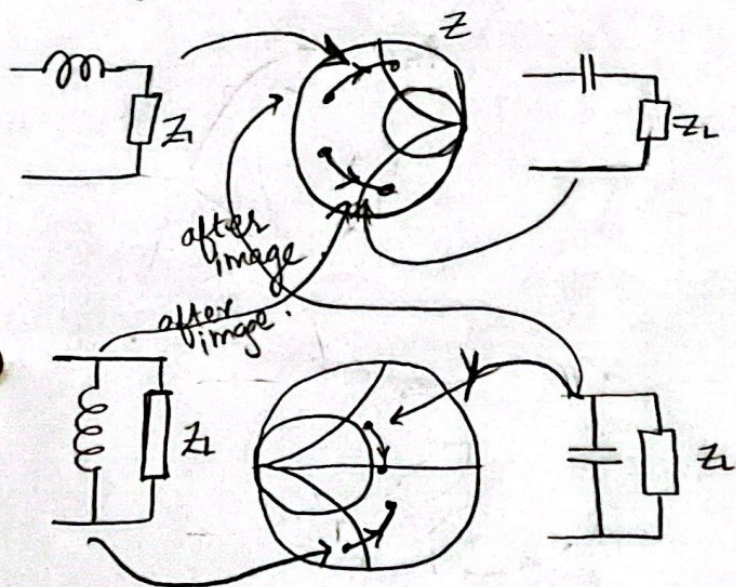
> Always move clockwise in a Smith Chart.



Move along constant VSWR circle in clockwise direction when extending the line length (electrical length).


Z series or shunt $\Rightarrow$ $\uparrow$ move up in Z or Y

C series or shunt $\Rightarrow$ $\downarrow$ move down in Z or Y





Impedance Matching

$$Z_L = Z_g^*$$

$$\Rightarrow T_L = T_g^*$$

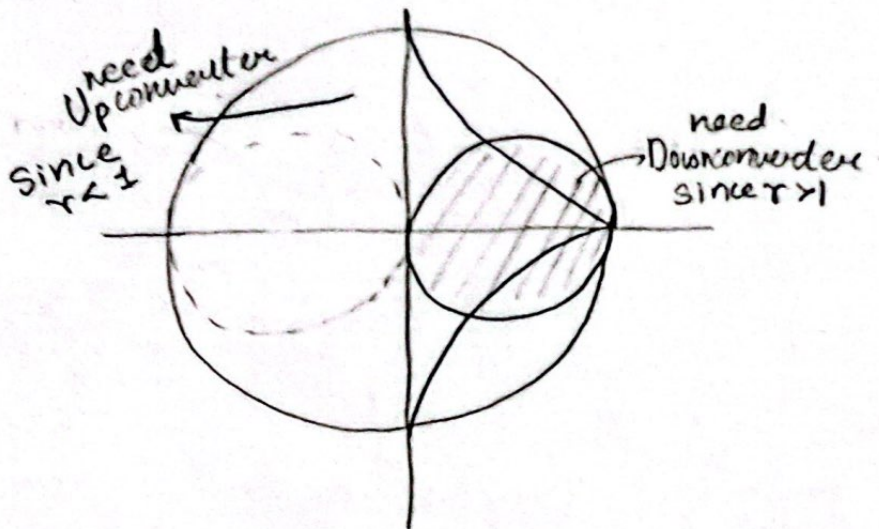

Upconversion.

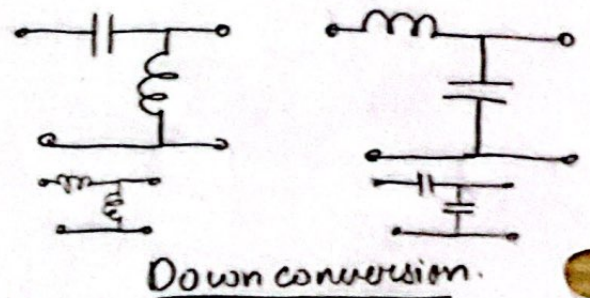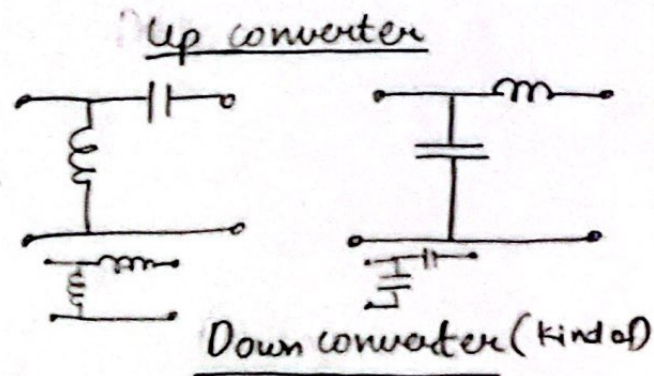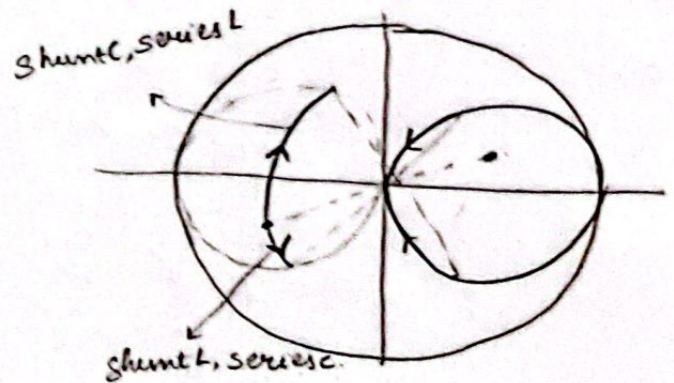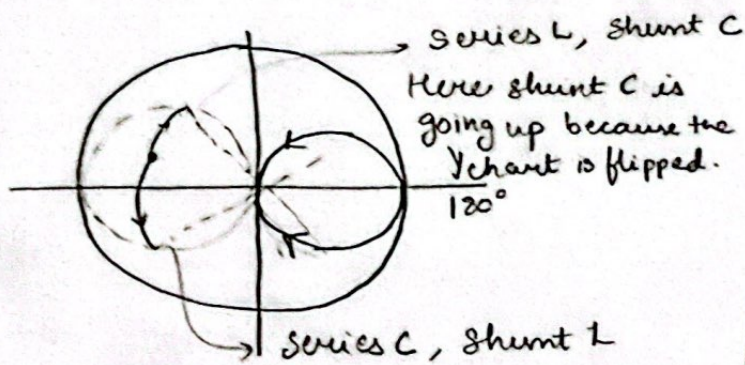

→ When dealing with shunts take mirror image w.r.t origin









→ Remember to renormalize correctly in the end.

→ The "Downconverter" Circuits can also upconvert some circuits as shown on Page 9.









Allowed regions

→ Shaded
up converters

reach this line

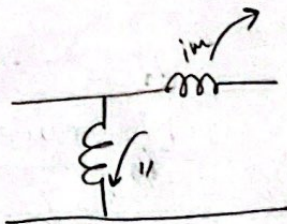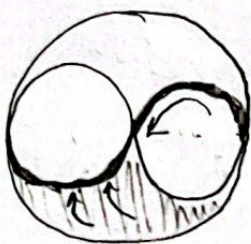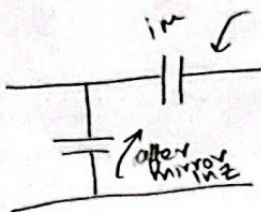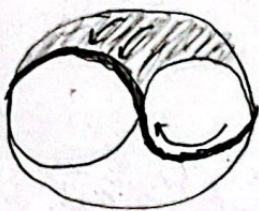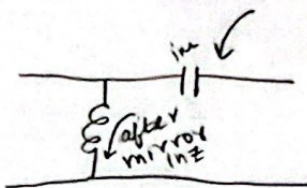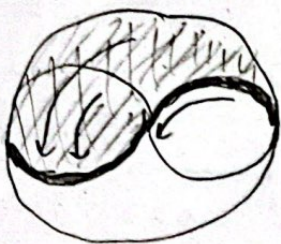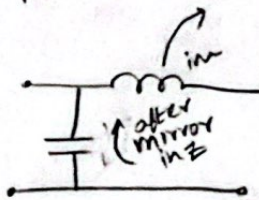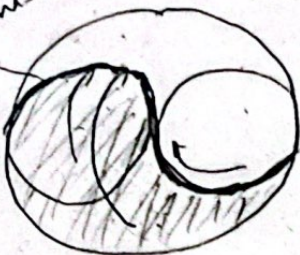


(Kind of)
Downconverters

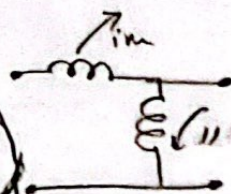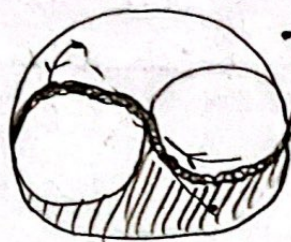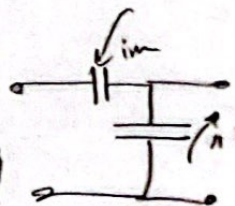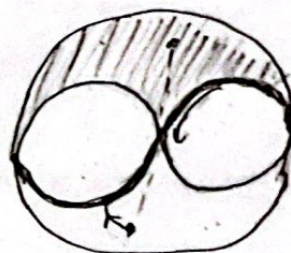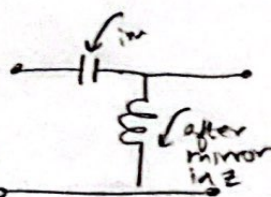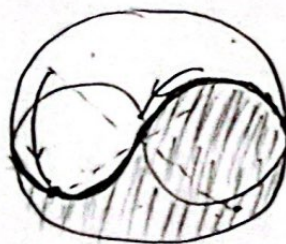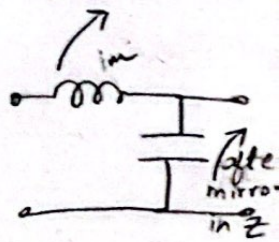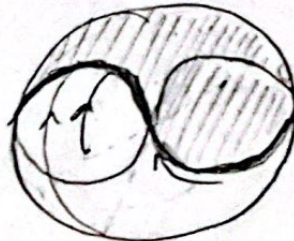


Matching using transmission lines

- MOVE along constant VSWR circle clockwise.
- stub moves exactly like shunt capacitor ^{or shunt inductor} _{after mirror}
- Z_0 is high and length is short $\Rightarrow$ T.L acts as an inductor with $L = \frac{Z_0 l}{u_p}$. Regardless of load Z_L as long as $Z_0 = Z_1 \rightarrow 3|Z_L|$

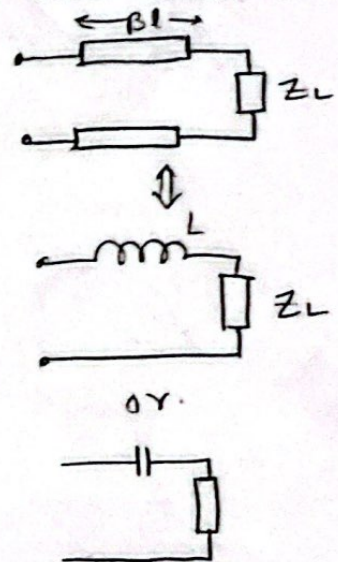

- Z_0 is low & length is short $\Rightarrow$ $C = \frac{l}{Z_0 u_p}$ $Z_1 = Z_0 < 3|Z_L|$

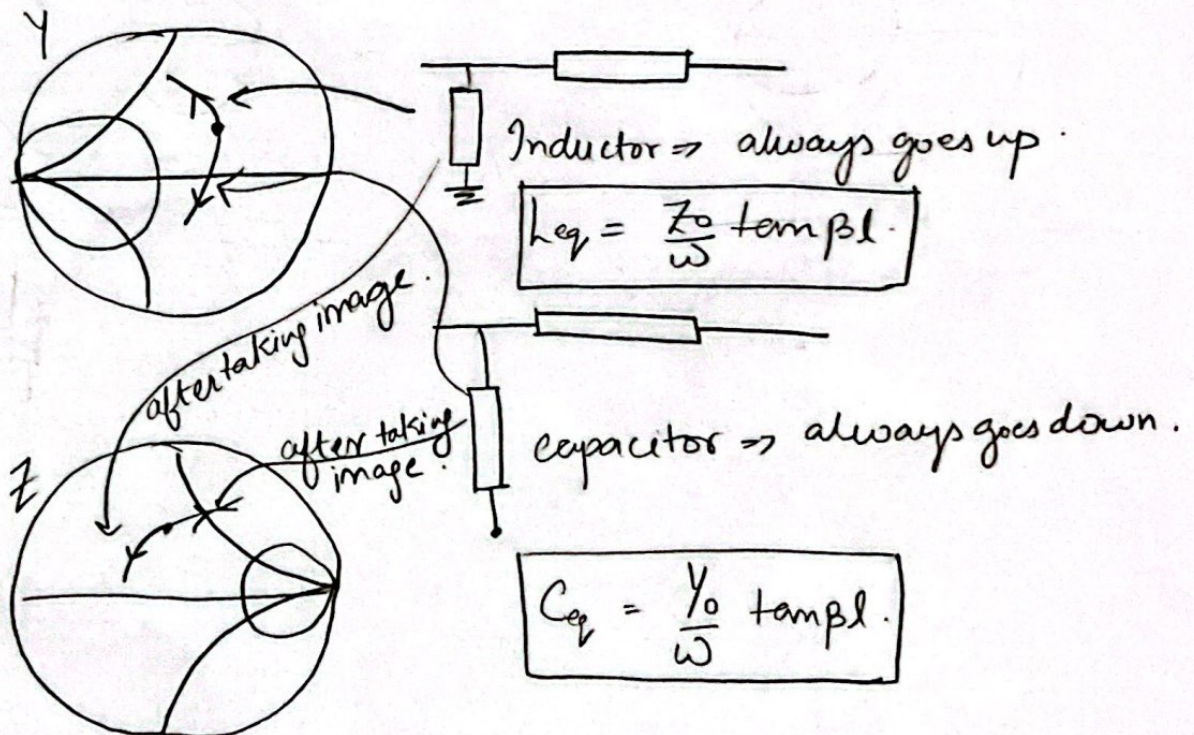- For Tline stub matching use Z/Y chart (preferred)




Lumped Elements and Lines

Inductors are the issue

$$Q = \frac{X}{R} = \frac{\text{Im}(Z)}{\text{Re}(Z)} = \frac{\text{Energy stored}}{\text{Power loss/cycle}}$$



> Equivalent model

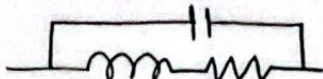

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$



$f < f_R \Rightarrow$ inductor

$f > f_R \Rightarrow$ capacitor

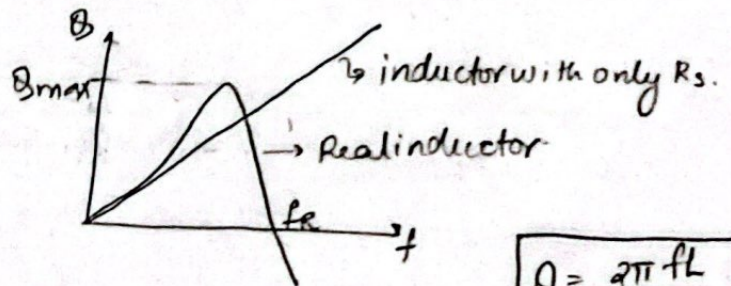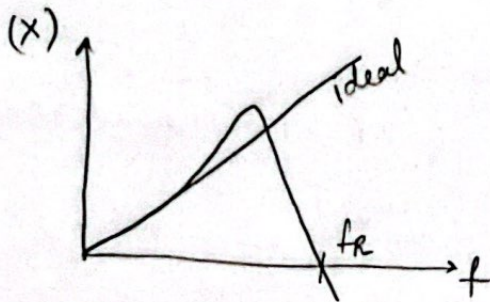

$$Q = \frac{2\pi fL}{R}$$

Integrated inductor model

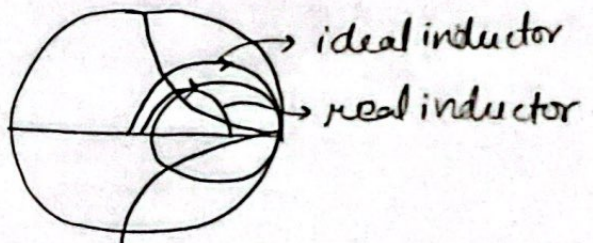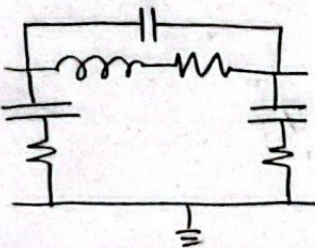

> At high frequency we can use a line of wire of length l & diameter d . Inductance is empirically given by.


$$L = 0.002l \left[\log\left(\frac{4l}{d}\right) - 1 \right] \mu\text{H}$$

→ Capacitors

model: $R_{eq} - C - L$


R is a function of frequency.
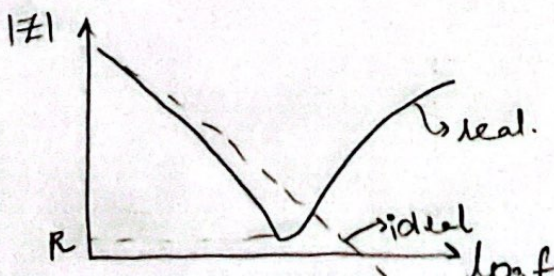
$$Q = \frac{1}{2\pi fRC} \quad f_R = \frac{1}{2\pi\sqrt{LC}}$$



Transmission lines and waveguides

Parallel plate TRL

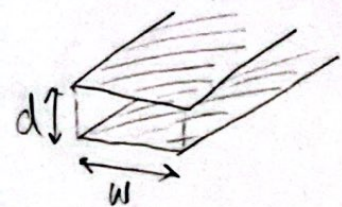

Assume $w \gg d$.

$$Z_0 = \sqrt{\frac{L}{C}} = \frac{\sqrt{\mu\epsilon}}{C} = \frac{1}{v_p C}$$

$$C = \epsilon \frac{w}{d} \Rightarrow$$

$$Z_0 = \sqrt{\frac{d}{w}}$$

Characteristic wave impedance of the medium b/w plates.

From Pozar

Transverse Electro Magnetic Waves.

> For TEM, at least 2 conductors must be used ($\Rightarrow$ no waveguides)

> $K_c = K^2 - \beta^2$ is the cut off wave number, $\boxed{K = \beta} \Rightarrow \underline{K_c = 0}$

$$\therefore \beta = K = \omega \sqrt{\mu\epsilon}$$

> The E field, H field & scalar potential ϕ satisfy Laplace's Equation. Therefore the transverse fields are like static fields.

> TEM modes have a well defined voltage, current & Z_0 for the structure.

$$> Z_{TEM} = \frac{E_x}{H_y} = \frac{\omega \mu}{\beta} = \sqrt{\frac{\mu}{\epsilon}} = \eta \quad \text{or} \quad Z_{TEM} = -\frac{E_y}{H_x} = \sqrt{\frac{\mu}{\epsilon}} = \eta$$

$$\therefore \vec{h}(x,y) = \frac{1}{Z_{TEM}} \hat{z} \times \vec{e}(x,y).$$

> Z_0 relates V, I travelling on the line & is a fn of both geometry and material.

> η or Z_{TEM} relates field components & is only a fn of material.

TE Mode

$$E_z = 0; H_z \neq 0$$

$\beta = \sqrt{k^2 - k_c^2}$ is a fn of frequency and geometry.

$$Z_{TE} = \frac{k\eta}{\beta} = \frac{\omega\mu}{\beta}$$

fn of freq.


H field now satisfies Helmholtz & is a travelling wave in z direction.

TM mode.

$$E_z \neq 0, H_z = 0, \beta = \sqrt{k^2 - k_c^2}$$

$$Z_{TM} = \frac{\beta}{\omega\epsilon} = \frac{\beta\eta}{k}$$

① Parallel Plate Waveguide.

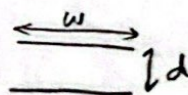

TEM modes

$$\vec{E} = -\hat{y} \frac{V_0}{d} e^{-jkz}$$

$$\vec{H} = \hat{z} \frac{V_0}{\eta d} e^{-jkz} \quad \text{potential on top plate} \quad k = \omega\sqrt{\mu\epsilon}$$

$$V = V_0 e^{-jkz}; I = \frac{\omega V_0}{\eta d} e^{-jkz}; Z_0 = \frac{\eta d}{\omega}; V_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{\mu\epsilon}}$$

$$\alpha_d = \frac{k \tan \delta}{2} \text{ Np/m} \quad \text{dielectric attenuation} \quad ; \quad \alpha_c = \frac{R_s}{\eta d}$$

TM modes

$$k_c = \frac{n\pi}{d}, \quad n = 0, 1, 2, 3, \dots$$

$$\beta = \sqrt{k^2 - \left(\frac{n\pi}{d}\right)^2}$$

$$E_z = A_n \sin \frac{n\pi y}{d} e^{-j\beta z} \quad H_x = \frac{j\omega\epsilon}{k_c} A_n \cos \frac{n\pi y}{d} e^{-j\beta z}$$

$$E_y = -\frac{j\beta}{k_c} A_n \cos \frac{n\pi y}{d} e^{-j\beta z} \quad E_x = H_y = 0.$$

n=0

$\Rightarrow TM_0 \Rightarrow E_z = 0 \rightarrow$ Identical to TEM mode.

→ $k > k_c \Rightarrow \underline{\beta \text{ is real}}$. $k = \omega \sqrt{\mu \epsilon} \Rightarrow f_c$ corresponding to k_c is the cut off frequency below which $k < k_c \Rightarrow \beta$ is imaginary $\Rightarrow$ evanescent modes & no power propagates.

$$f_c = \frac{k_c}{2\pi\sqrt{\mu\epsilon}} = \frac{n}{2d\sqrt{\mu\epsilon}}$$


Dominant mode = TM1 @ $f_c = \frac{1}{2d\sqrt{\mu\epsilon}}$

$$Z_{TM} = -\frac{E_y}{H_x} = \frac{\beta}{\omega\epsilon} = \frac{\beta\eta}{k} \rightarrow \text{real when } k > k_c.$$

$$v_p = \frac{\omega}{\beta} > \frac{\omega}{k} \Rightarrow v_p > c$$

$$\lambda_g = \frac{2\pi}{\beta} \rightarrow \begin{matrix} \text{guide wavelength} \\ \text{distance b/w equiphase planes.} \end{matrix}$$
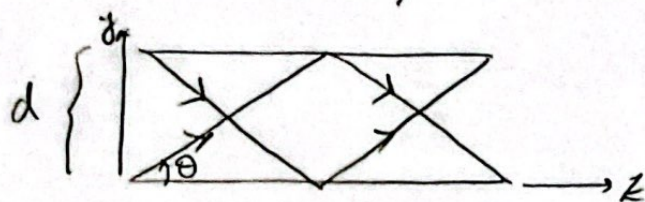
> Could be interpreted as a pair of bouncing planewaves.



At $f = f_c$ $\theta = 90^\circ \Rightarrow$ no propagation.

Phase velocity of each planewave along $z = \frac{1}{\sqrt{\mu\epsilon} \cos \theta} > c$.

$$\alpha_c = \frac{2\omega\epsilon R_s}{\beta d} = \frac{2kR_s}{\beta\eta d}.$$

TE modes

> β, f_c are same.


$$Z_{TE} = \frac{E_x}{H_y} = \frac{k\eta}{\beta}$$

There is no TE₀ mode.

TE₁ & TM₁ occur at the same frequency.

II Rectangular Waveguide

> No TEM.

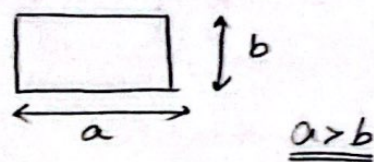

TE Modes.

$$\beta = \sqrt{k^2 - k_c^2} = \sqrt{k^2 - \left(\frac{m\pi}{a}\right)^2 - \left(\frac{n\pi}{b}\right)^2}$$

$$k > \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2} \Rightarrow \text{propagation!}$$

$$f_{cmn} = \frac{1}{2\pi\sqrt{\mu\epsilon}} \sqrt{\left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2}$$

> Since $a > b$, TE₁₀ occurs at the lowest frequency & is dominant

> There is no TE₀₀ mode.

$$Z_{TE} = \frac{k\eta}{\beta} \quad ; \quad \lambda_g = \frac{2\pi}{\beta} > \frac{2\pi}{k} = \lambda \quad \text{wavelength of plane wave in the same medium.}$$

$$\text{TE}_{10}: k_c = \frac{\pi}{a}; \beta = \sqrt{k^2 - \left(\frac{\pi}{a}\right)^2}$$

TM modes

> β & f_{cmn} are identical.

> However there are no TM₀₀, TM₁₀, TM₀₁ modes (due to the E, H formulae).
So lowest TM mode is TM₁₁ & therefore TE₁₀ is the dominant mode.

$$Z_{TM} = \frac{\beta\eta}{k}$$

● First five modes: TE₁₀, TE₂₀, TE₀₁, TE₁₁, TM₁₁.

$$\alpha_d = \frac{k^2 + \tan\delta}{2\beta} N_p/m \quad ; \quad \alpha_c = \frac{R_s}{a^3 b \beta k \eta} (2b\pi^2 + a^3 k^2)$$

III Circular Waveguide.

Solutions to Helmholtz' or Laplace's equations in cylindrical coordinates gives Bessel's functions of integer order.

Bessel Equation: $\rho^2 \frac{d^2 R}{d\rho^2} + \rho \frac{dR}{d\rho} + (\rho^2 k_c^2 - k^2 \rho^2) R = 0.$

TE modes.

$$k_{cnm} = \frac{P'_{nm}}{a}$$

roots of $J'_n(x)$ s.t. P'_{nm} is the m^{th} root of J'_n
 $J'_n(x)$ is the derivative of $J_n(x)$ → Bessel fn of first kind.

$$\beta_{nm} = \sqrt{k^2 - k_{cnm}^2} \quad f_{cnm} = \frac{k_{cnm}}{2\pi\sqrt{\mu\epsilon}}$$

> TE₁₁ is the dominant mode, (it has the smallest P'_{nm})

> There is no TE₁₀ mode, but there is a TE₀₁ mode.

$$Z_{TE} = \frac{\eta k}{\beta}$$

TM modes.

$$k_c = \frac{P_{nm}}{a}$$



mth root of $J_n(x)$

$$\beta_{nm} = \sqrt{k^2 - k_c^2}$$

$$Z_{TM} = \frac{\eta \beta}{k} \quad f_{cnm} = \frac{k_c}{2\pi\sqrt{\mu\epsilon}}$$

> First TM mode is TM₀₁ & comes after TE₁₁.
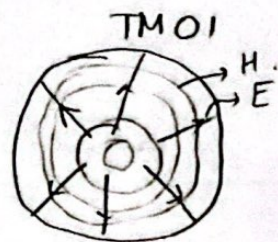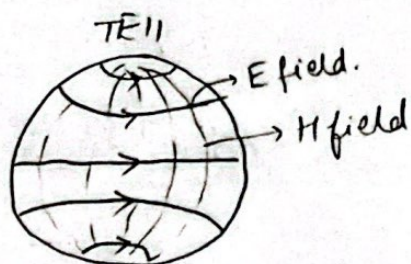
> Attenuation of TE₀₁ is very low @ high freq, but it excites other modes.



IV

Coaxial line.



$\phi(r, \phi) = \frac{V_0 \ln(b/r)}{\ln(b/a)}$ for TEM mode.


Higher order modes.

- > Hard to analyze.
- > TE₁₁ is the dominant waveguide mode.
- > $k_c = \frac{2}{a+b}$ - empirical equation.

V

Surface waves on a Grounded Dielectric Sheet

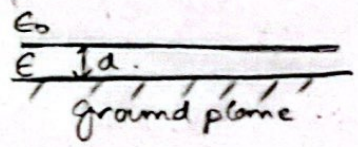TM: $f_c = \frac{nc}{2d\sqrt{\epsilon_r - 1}}$ → cut off for TM_n where $n > 0$




- > TM₀ is dominant & has 0 cut off freq. & therefore always exists.

TE: > No TE₀ exists. For $n > 0$ $f_c = \frac{(2n-1)c}{4d\sqrt{\epsilon_r - 1}}$

Order of modes: TM₀, TE₁, TM₁, TE₂, TM₂...


VI Stripline.

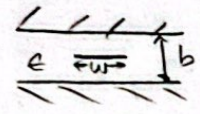

TEM: $v_p = c/\sqrt{\epsilon_r}$; $\beta = \frac{\omega}{v_p} = \sqrt{\epsilon_r} k_0$ $Z_0 = \frac{1}{v_p G} = \sqrt{\frac{L}{C}}$

There are empirical formula for L, C. Check Pozar Pg. 142.

VII Microstripline.

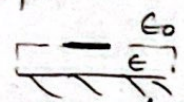


Partial dielectric ⇒ v_p is different in

- dielectric & air ⇒ cannot use phase matching ⇒ No TEM, only quasiTEM
- $1 < \epsilon_e < \epsilon_r$, where ϵ_e is the effective permittivity.
- Empirical formulae for ϵ_e , Z_0 , $\frac{W}{d}$, α_c are in Pozar Pg 148
- $v_p = c/\sqrt{\epsilon_e}$; $\beta = k_0 \sqrt{\epsilon_e}$

Back to lecture Notes

Microstrip lines

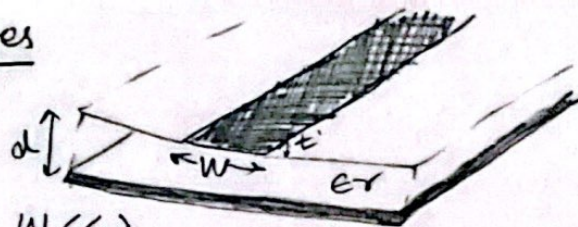

Assume $W \gg d$; $W \ll \lambda$

$$u_p = \frac{u_c}{\sqrt{\epsilon_e}} \rightarrow \text{speed of light } 3 \times 10^8 \text{ m/s}, \quad 1 \leq \epsilon_e \leq \epsilon_r$$


$$Z_0 = \frac{Z_{0\text{air}}}{\sqrt{\epsilon_e}} \rightarrow Z_0 \text{ when dielectric is air}$$

$$\epsilon_e = \epsilon_r \text{ if } W \gg d.$$

$$\epsilon_e \approx \frac{1}{2}(\epsilon_r + 1) \text{ if } W \ll d.$$


Guide wavelength
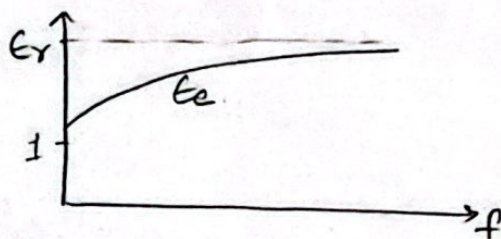
$$\lambda_g = \frac{\lambda_0}{\sqrt{\epsilon_e}}$$



Filling Factor (portion of EM energy inside the substrate)
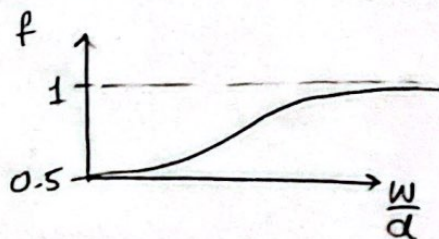
$$f = \frac{\epsilon_e - 1}{\epsilon_r - 1} \quad \begin{matrix} \frac{1}{2} < f < 1 \\ (W \ll d) & (W \gg d) \end{matrix}$$



Dielectric loss.

$$\gamma = \sqrt{j\omega\mu(\sigma + j\omega\epsilon)}$$

$$= \underbrace{j\omega\sqrt{\mu\epsilon}}_{j\beta} \sqrt{1 - j\frac{\sigma}{\omega\epsilon}}$$

$$\gamma \approx \underbrace{\frac{1}{2}\sigma\sqrt{\frac{\mu}{\epsilon}}}_{\alpha} + j\omega\sqrt{\mu\epsilon}_{\beta}$$

Loss tangent

$$\tan \delta = \frac{\sigma}{\omega\epsilon}$$

Conductance $G = \omega C \tan \delta$.

For low loss line.

$$\alpha = \alpha_c + \alpha_d = \frac{1}{2} R \sqrt{\frac{C}{L}} + \frac{1}{2} G \sqrt{\frac{L}{C}} \quad ; \quad \alpha_d = \frac{1}{2} G \sqrt{\frac{L}{C}}$$

$$\alpha_d = \frac{Z_0}{2} \omega C \tan \delta$$

$$f_d = \frac{\epsilon_r}{\epsilon_e} f = \frac{\epsilon_r}{\epsilon_e} \left(\frac{\epsilon_e - 1}{\epsilon_r - 1} \right)$$

$$\alpha_d = \frac{\omega}{2} \sqrt{\mu_0 \epsilon_0} \sqrt{\epsilon_e} \tan \delta \quad \text{Np/m}$$


$$\alpha_d = \frac{\omega}{2} \sqrt{\mu_0 \epsilon_0} \sqrt{\epsilon_e} \frac{\epsilon_r}{\epsilon_e} \left(\frac{\epsilon_e - 1}{\epsilon_r - 1} \right) \tan \delta$$

Thinnes continued.

Skin depth.


$$\delta_s = \frac{1}{\sqrt{\pi f \mu \sigma}}$$

$$\alpha_c = \sqrt{\pi f \mu \sigma}$$

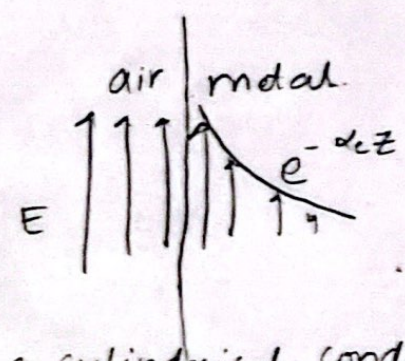


DC resistance $R_{dc} = \frac{1}{\sigma} \frac{L}{\pi r^2}$ of a cylindrical conductor
 $L \rightarrow$ length, $r \rightarrow$ radius

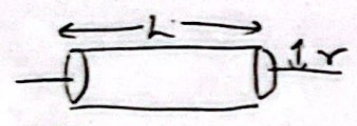RF resistance $R_{RF} = \frac{1}{\sigma} \frac{L}{2\pi r \delta_s}$



For a sheet

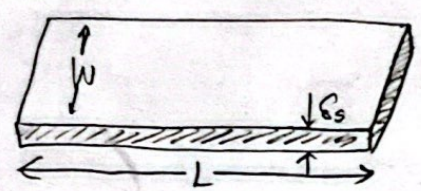

$$R_s = \sqrt{\frac{W \mu_0}{2 \sigma}}$$

$R = \frac{1}{\sigma} \frac{L}{W \delta_s}$ since $R = \frac{\rho L}{A}$

Let $R_s = \frac{1}{\sigma \delta_s}$ is the sheet resistance

We know $\delta_s = \frac{1}{\sqrt{\pi f \mu \sigma}}$ since current only flows in this depth & not in the real depth.

$\times R = R_s \frac{L}{W}$

Conductor loss α_c in Microstripline.

$$\alpha_c = \frac{R_s}{2 Z_0 W}$$

If skin is rough.

$$\alpha'_c = \alpha_c \left[1 + \frac{2}{\pi} \tan^{-1} \left(1.4 \frac{\Delta}{\delta_s} \right) \right]$$

rms surface roughness

Power.

Power at some point $P = P_0 e^{-2\alpha z}$ $\rightarrow$ Attenuates fast as a fn of α .

$\rightarrow$ Wide line $\Rightarrow$ low Z_0 & low loss since $Z_0 = \frac{1}{\epsilon_p c}$

$\rightarrow$ Choose $h < \frac{\lambda_g}{4}$ & $W < \frac{\lambda_g}{2}$ to prevent excitation of higher order modes.

Network Analysis

$$[V] = [Z][I]$$

$n \times 1 \quad n \times n \quad n \times 1$

$$[I] = [Y][V]$$

$$\text{and } [Z] = [Y]^{-1}$$


Reciprocal $\Rightarrow Z_{ij} = Z_{ji}$ or $Y_{ij} = Y_{ji}$

Lossless $\Rightarrow Z, Y$ are purely imaginary

Scattering Matrix

$$a_j = \frac{V_j^+}{\sqrt{Z_0}}$$

$$b_j = \frac{V_j^-}{\sqrt{Z_0}}$$

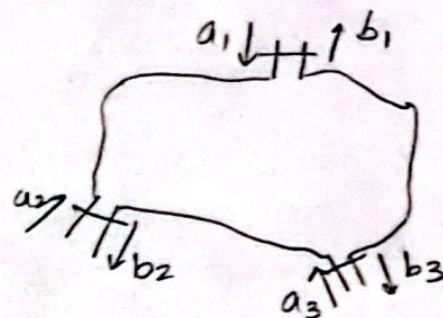

$$[b] = [S][a]$$

Reciprocal $\Rightarrow S_{ij} = S_{ji}$

Lossless $\Rightarrow [S]^T [S] = I \Rightarrow \text{Sum of squares of columns} = 0.$

$$P_{\text{loss}} = 1 - |S_{11}|^2 - |S_{21}|^2 - |S_{31}|^2$$

$\hookrightarrow$ Fraction of power lost to network.

Return loss

$$RL = -20 \log |S_{11}| \text{ dB}$$

Insertion loss

$$IL = -20 \log |S_{21}| \text{ dB}$$

Insertion gain

$$IG = 20 \log |S_{21}| \text{ dB}$$

Mismatch loss

$$ML = -10 \log [1 - |S_{11}|^2]$$

Power in dBm

$$= +10 \log (\text{Power in mWatt})$$

Γ

VSWR

Reflected power(%)

0.89

17.4

79.4

~ 0.708

~ 5.85

50%

~ 0.32

~ 1.92

10%

high $\Rightarrow$ good match

RL (dB)

ML (dB)

1 dB

6.87 dB


3 dB

3 dB


10 dB

$\sim 0.45 \text{ dB}$


S parameters cond.

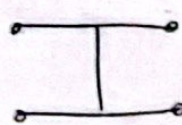

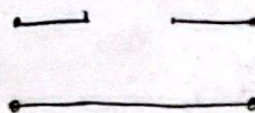
$$\Rightarrow [S] = \begin{bmatrix} -1 & 0 \\ 0 & -1 \end{bmatrix}$$


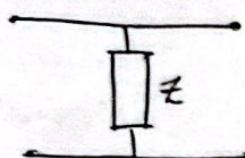
$$[S] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$



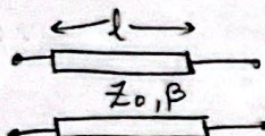
$$[S] = \begin{bmatrix} \frac{-Z_0}{2Z+Z_0} & \frac{2Z}{2Z+Z_0} \\ \frac{2Z}{2Z+Z_0} & \frac{-Z_0}{2Z+Z_0} \end{bmatrix}$$





$$[S] = \begin{bmatrix} 0 & e^{-j\beta l} \\ e^{-j\beta l} & 0 \end{bmatrix}$$

Shift in reference plane.
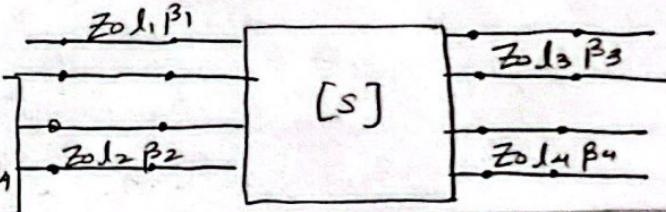
$$[S'] = \begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_4} \end{bmatrix} [S] \begin{bmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_4} \end{bmatrix}$$

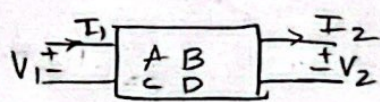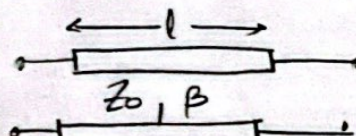
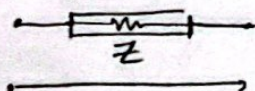
ABCD parameters

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


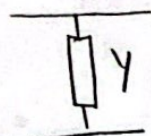


$$\Rightarrow [A] = \begin{bmatrix} \cos \beta l & j Z_0 \sin \beta l \\ j Y_0 \sin \beta l & \cos \beta l \end{bmatrix}$$

Reciprocal $\Rightarrow \boxed{AD - BC = 1}$




$$A = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$



$$A = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

S matrix of lossless T junction.

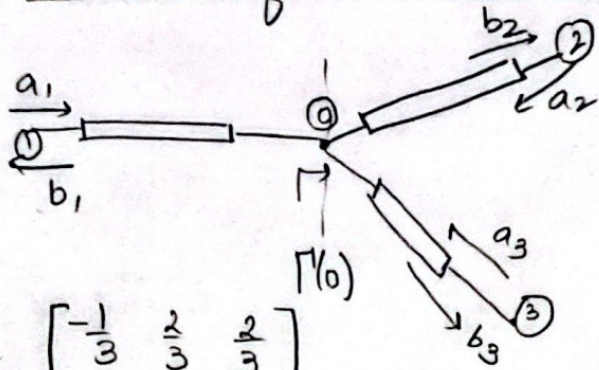

$$[S] = \begin{bmatrix} -\frac{1}{3} & \frac{2}{3} & \frac{2}{3} \\ \frac{2}{3} & -\frac{1}{3} & \frac{2}{3} \\ \frac{2}{3} & \frac{2}{3} & -\frac{1}{3} \end{bmatrix}$$


Assuming lengths are equal.

$$\Gamma(0) = -\frac{1}{3}$$


$a_1 + b_1 = a_2 + b_2 = a_3 + b_3$ since the lengths are same & the waves must be equal at ①.

Circulator $\Rightarrow$ nonreciprocal.

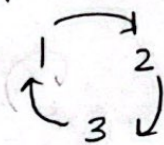
$$S = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$


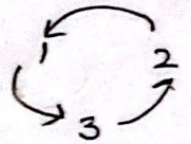
$$S = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \end{bmatrix}$$



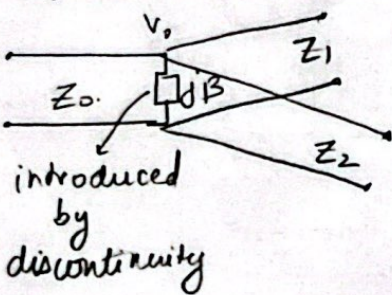T-junction power divider. (not matched). Lossless & reciprocal.



$$P_{in} = \frac{1}{2} \frac{V_0^2}{Z_0}$$


$$P_1 = \frac{1}{2} \frac{V_0^2}{Z_1}$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_2}$$

$$\underline{3dB} \Rightarrow P_1 = P_2 = P_{in} \Rightarrow Z_1 = Z_2 = 2Z_0.$$

$\Rightarrow$ Input alone is matched but no isolation.

T-junction loss divider.

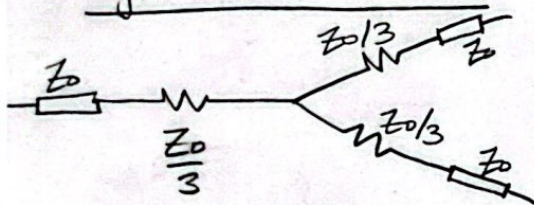

$$S = \begin{bmatrix} 0 & \frac{1}{2} & \frac{1}{2} \\ \frac{1}{2} & 0 & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} & 0 \end{bmatrix}$$

$\rightarrow$ 6dB insertion loss.

$\rightarrow \frac{1}{4}$ power split b/w g/p's & $\frac{1}{2}$ power dissipated.

$\Rightarrow$ High bandwidth.


$\rightarrow$ measurement devices.

Wilkinson Power Divider

$$[S] = \begin{bmatrix} 0 & \frac{-j}{\sqrt{2}} & \frac{-j}{\sqrt{2}} \\ \frac{-j}{\sqrt{2}} & 0 & 0 \\ \frac{-j}{\sqrt{2}} & 0 & 0 \end{bmatrix}$$

- All ports are matched.
- lossless only for power injected to port ① or to both ② & ③ equally.
- Reciprocal.

→ Insertion loss = 3dB.

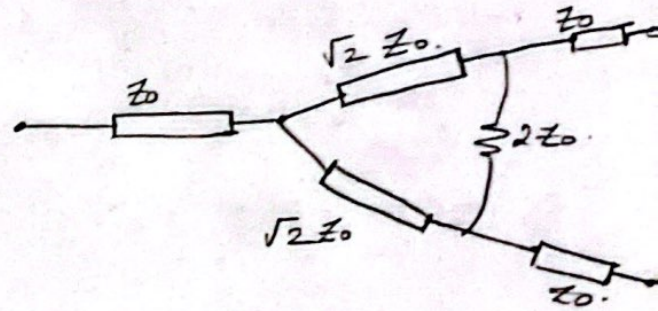

Four Port Networks

Coupling factor $C = -20 \log |S_{31}| \text{ dB}$

Directivity $D = 20 \log \frac{|S_{31}|}{|S_{41}|} \text{ dB}$

→ determines how well coupled & reflected waves are isolated.


Ideal coupler $\rightarrow S_{41} = 0 \rightarrow D = \infty$

Isolation $I = -20 \log |S_{41}| \text{ dB}$


RL = $-20 \log |S_{11}| \text{ dB}$

IL = $-20 \log |S_{12}| \text{ dB}$ or $-20 \log |S_{21}| \text{ dB}$.

$$I = D + C \text{ in dB}$$

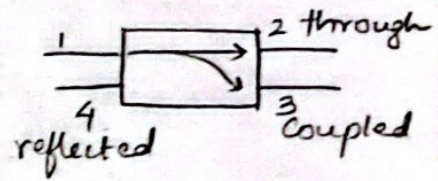


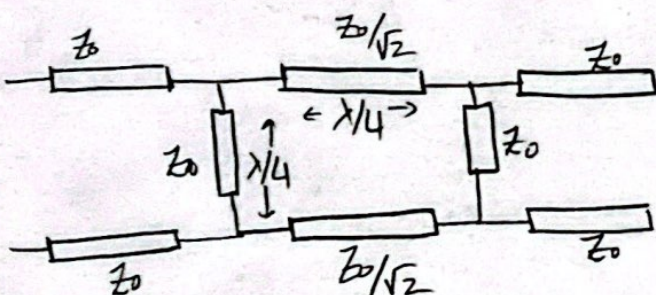Branched line Coupler [3dB Hybrid coupler]



$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

Rot race coupler.

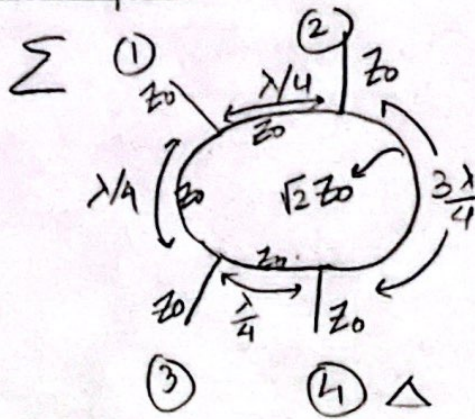


$$[S] = \frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

→ Inputs to ② & ③ → Σ at ① & Δ at ④


Applications of BLC.

Matched switches.

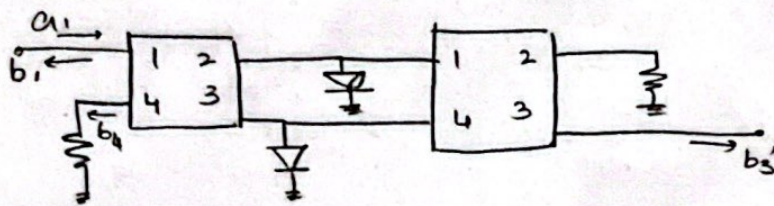


→ b_1 is always 0 regardless of open or closed diodes.

Wideband amplifier

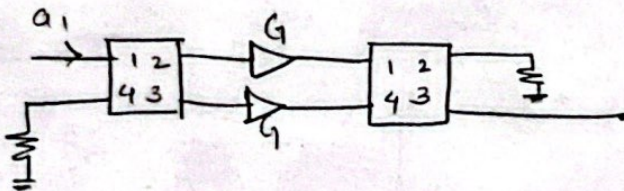

Reflection type phase shifter.


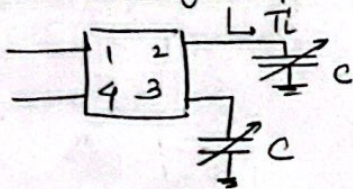


$$\angle S_{41} = -90^\circ + \angle \theta$$

$$T_L = 1/\theta$$

Coupled line Coupler.

Coupled.

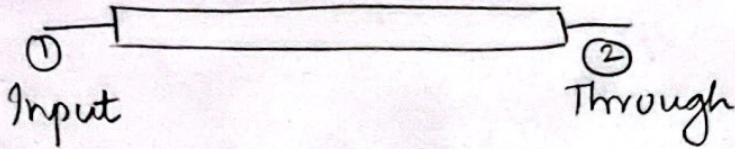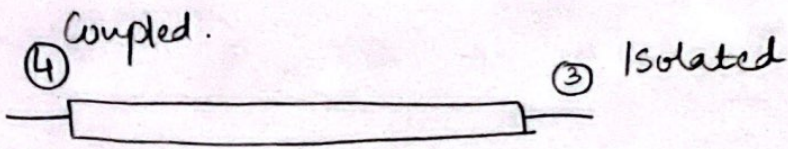 $Z_{oe} \rightarrow$ even mode Z_0 . $Z_{oo} \rightarrow$ odd mode impedance.

$$Z_0 = \sqrt{Z_{oe} Z_{oo}}$$

$$\text{Coupling factor } C = \frac{Z_{oe} - Z_{oo}}{Z_{oe} + Z_{oo}} \Rightarrow Z_{oe} = Z_0 \sqrt{\frac{1+C}{1-C}} \quad Z_{oo} = Z_0 \sqrt{\frac{1-C}{1+C}}$$

$$S_{11} = S_{22} = S_{33} = S_{44} = 0$$

$$S_{21} = -j\sqrt{1-C^2}$$

$$S_{31} = C$$

$$S_{41} = 0$$

At the design frequency $\Rightarrow \theta = \frac{\pi}{2}$

Diodes.


> Schottky diodes are commonly used.

$$I(V) = I_s (e^{\alpha V} - 1) \quad \text{where } \alpha = \frac{q}{n k T}$$

> PIN diodes (P-type - Intrinsic - N type).

Forward bias $\Rightarrow$

Reverse bias $\Rightarrow$

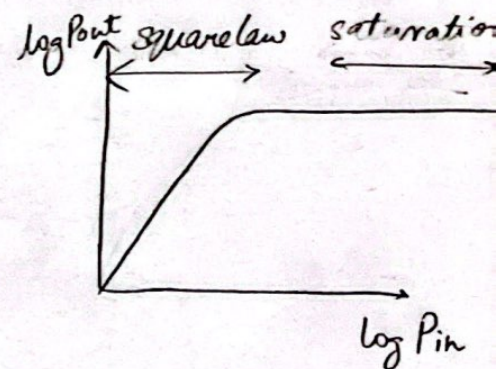

- > Single pole reflective switch
 - > Single pole double throw
 - > Switched line phase shifter.
- } Common applications.

Noise

Thermal noise

RMS value of thermal noise across resistor:

$$V_n = \sqrt{\frac{4hfBR}{e^{hf/KT} - 1}}$$

$h = 6.626 \times 10^{-34} \text{ Js}$ → Planck's const.

$k = 1.38 \times 10^{-23} \text{ J/K}$ → Boltzmann's const.

f → center freq

B → BW

At microwave freq. $hf \ll kT$


$$\Rightarrow V_n = \sqrt{4kTBR}$$

$$\text{Available thermal noise power} = P_n = \frac{V_L^2}{R} = \frac{(V_n/2)^2}{R} = \frac{V_n^2}{4R}$$

$$\Rightarrow P_n = kTB$$

At room temp. (290 K)

$$P_n = -174 \text{ dBm} + 10 \log B$$

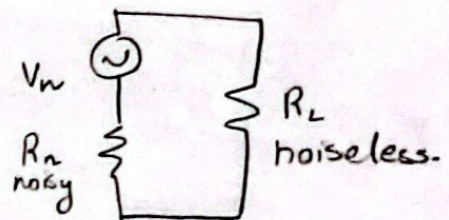

Equivalent noise temperature → (sensitive scale used in astronomy)

A resistor at T_e produces the same noise as our noise source with a gain of G & BW $\rightarrow B$.

$$N_o = (kT_e B) G$$

$$\Rightarrow T_e = \frac{N_o}{kGB}$$

Noise figure

$$F = \frac{S_i/N_i}{S_o/N_o} \geq 1$$

$$NF = 10 \log F$$

$$T_e = (F-1)T_o$$

not in dB

Cascaded noise figure

$$F_{\text{case}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} + \frac{F_4 - 1}{G_1 G_2 G_3} + \dots$$

nothing is in dB.

→ Noise figure of a matched lossy network is equal to its loss in dB at room temperature.

→ N.F of attenuator = Insertion loss in dB.

→ If the reference temperature of attenuator $\neq T_0$

$$NF = 1 + \frac{(L-1)T}{T_0} \rightarrow \text{loss.}$$

L N A Design.

Noise figure of a two port network.

$$F = F_{min} + \frac{R_N}{G_s} |Y_s - Y_{opt}|^2$$

$$Y_s = G_s + jB_s$$

$R_N \rightarrow$ equivalent noise resistance.

$Y_s \rightarrow$ source admittance.

$Y_{opt} \rightarrow$ optimum source resistance to minimize $F \rightarrow F_{min}$.

$$Y_{opt} = \frac{1}{Z_0} \cdot \frac{1 - \Gamma_{opt}}{1 + \Gamma_{opt}}$$

$$\Rightarrow F = F_{min} + \frac{4R_N}{Z_0} \frac{|\Gamma_s - \Gamma_{opt}|^2}{(1 - |\Gamma_s|^2)(1 + |\Gamma_{opt}|^2)}$$

For a constant F , the equation describes a circle in Γ plane.

$$\text{Center: } C_F = \frac{\Gamma_{opt}}{N+1}$$


$$\text{Radius: } R_F = \frac{\sqrt{N(N+1 - |\Gamma_{opt}|^2)}}{N+1}$$

where,

$$N = \frac{F - F_{min}}{4R_N/Z_0} |1 + \Gamma_{opt}|^2$$

Nonlinearity and Distortion - Dynamic Range.

Gain compression.

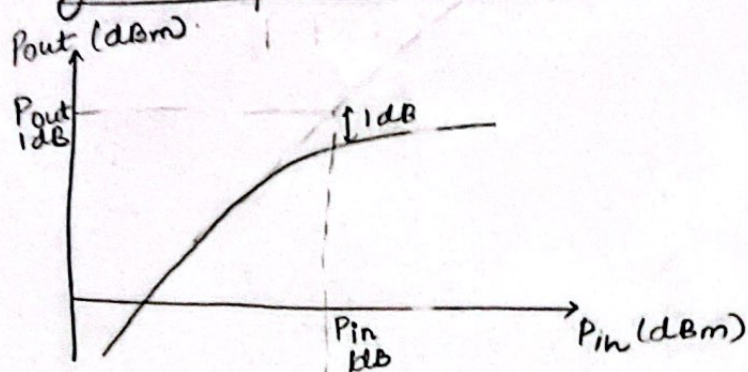

$$y(x) = K_1 f(x) + K_2 f^2(x) + K_3 f^3(x) + \dots$$

$$f(x) = A_1 \cos \omega_1 t$$

$$\Rightarrow y(x) = K_1 A_1 \cos \omega_1 t + K_2 A_1^2 \left(\frac{1 + \cos 2\omega_1 t}{2} \right) + K_3 \left[A_1^3 \left(\frac{3 \cos \omega_1 t}{4} \right) \right] + \dots$$

$$\Rightarrow \text{Gain at } \omega_1 = \frac{y(x) \text{ at } \omega_1}{f(x) \text{ at } \omega_1} = \frac{K_1 A_1 + K_3 A_1^3 (3/4)}{A_1}$$


$$\boxed{\text{Gain} = K_1 + K_3 \left(\frac{3}{4} A_1^2 \right)}$$

usually negative.

Intermodulation & Distortion.

2 tone test: $f(x) = A_1 \cos \omega_1 t + A_2 \cos \omega_2 t$ generates $2\omega_1 - \omega_2$ & $2\omega_2 - \omega_1$, that are in band.

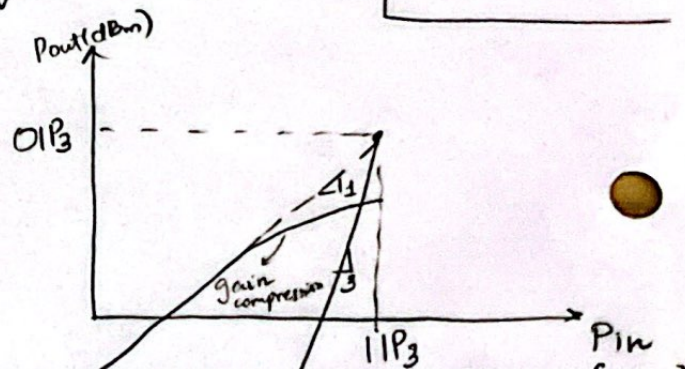If $A_1 \approx A_2$, At the output amplitude of IM terms is $\frac{3}{4} K_3 A_1^2$ & amplitude of the signal is $K_1 A_1$. Therefore IM terms grow very fast.




SFDR Spurious Free Dynamic Range.

$$\begin{aligned} \text{DR (in dB)} &= \frac{2}{3} [11P_3 \text{ (dBm)} - S_{\text{rmin}} \text{ (dBm)}] \\ &= \frac{2}{3} [11P_3 \text{ (dBm)} - N_o \text{ (dBm)}]_{\text{output noise}} \end{aligned}$$

Cascaded OIP3

$$\frac{1}{\text{OIP3}} = \frac{1}{\text{OIP3}_1 G_2 G_3} + \frac{1}{\text{OIP3}_2 G_3} + \frac{1}{\text{OIP3}_3}$$

Power Gain Definitions

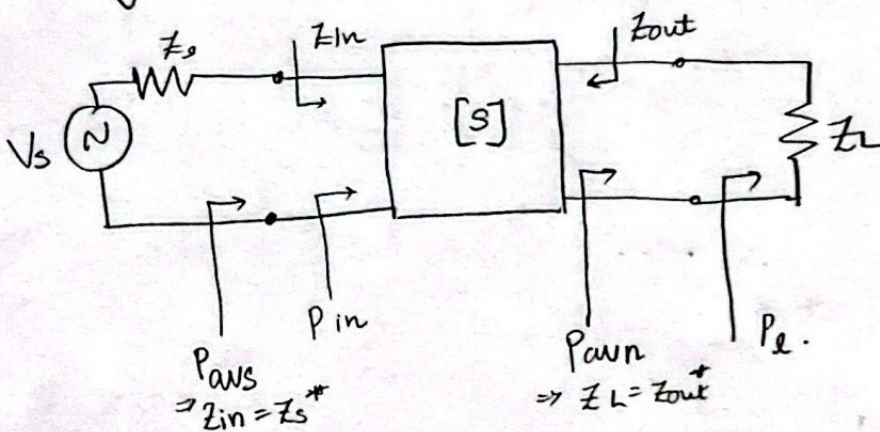

$$P_{\text{avs}} = \frac{V_s^2}{8 R_s}$$

$$\Gamma_{\text{in}} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{\text{out}} = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s}$$

$$P_{\text{in}} = \frac{|V_s|^2}{8 Z_0} \frac{|1 - \Gamma_s|^2}{|1 - \Gamma_{\text{in}} \Gamma_s|^2} (1 - |\Gamma_{\text{in}}|^2)$$

$$P_L = \frac{|V_s|^2}{8 Z_0} \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)^2 |1 - \Gamma_s|^2}{|1 - S_{22} \Gamma_L|^2 |1 - \Gamma_{\text{in}} \Gamma_s|^2}$$

$$P_{\text{avs}} = \frac{|V_s|^2}{8 Z_0} \frac{|1 - \Gamma_s|^2}{1 - |\Gamma_s|^2}$$

$$P_{\text{avn}} = \frac{|V_s|^2}{8 Z_0} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{\text{out}}|^2)}$$

Operating power gain (independent of Z_s)

$$G_P = \frac{P_L}{P_{in}} = \frac{1}{1 - |\Gamma_{in}|^2} |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2}$$

Available Power gain (independent of Z_L)

$$G_A = \frac{P_{avn}}{P_{avs}} = \frac{(1 - |\Gamma_S|^2)}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1}{(1 - |\Gamma_{out}|^2)}$$

Transducer Power gain (Depends on both Z_s & Z_L)

$$G_T = \frac{(1 - |\Gamma_S|^2)}{|1 - \Gamma_S \Gamma_{in}|^2} |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2}$$

→ $G_{Tmax} = G_T = G_A = G_P = G_{Amax} = G_{Pmax}$ if simultaneous conjugate matching.

→ Unilateral → $S_{12} = 0$

$$\Rightarrow G_{Tu} = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_S S_{11}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

RF Amplifier Design

$$G_T = G_S G_O G_L$$

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in} \Gamma_S|^2} \quad \text{gain contribution due to input matching}$$

$$G_O = |S_{21}|^2 \quad \text{device gain}$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} \quad \text{gain contribution due to output matching.}$$

$$\Gamma_{out} = S_{22}, \quad \Gamma_{in} = S_{11} \quad \text{if } S_{12} = 0 \rightarrow \text{unilateral.}$$

→ $|\Gamma_{in}|$ or $|\Gamma_{out}| > 1$ at some frequency $\Rightarrow$ potentially unstable!

Stability

a) Unconditional stability

● $|\Gamma_{in}| < 1$ & $|\Gamma_{out}| < 1$ for all possible source & load impedances

b) Conditional stability

$|\Gamma_{in}| < 1$ & $|\Gamma_{out}| < 1$ for some set of source & load impedances.

→ Unilateral device $\Rightarrow |S_{11}| < 1$ & $|S_{22}| < 1$

→ For bilateral device: Use stability circles.

loci in the Γ plane for which $|\Gamma_{in}| = 1$ or $|\Gamma_{out}| = 1$.

→ locus of Γ_L s to make $|\Gamma_{in}| = 1$ give output stability circles

$$\left| S_{11} + \frac{S_{21} S_{12} \Gamma_L}{1 - S_{22} \Gamma_L} \right| = 1$$

$$\bullet \text{ Let } \Delta = S_{11} S_{22} - S_{12} S_{21}$$

Output Stability Circles

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2}$$

$$R_L = \left| \frac{S_{12} S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

Input Stability Circles

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2}$$

$$R_S = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

> We know that the circle defines boundary of stability, but how do we know if inside or outside is stable?

Use $K \Delta$ test

An amplifier is unconditionally stable iff $K > 1$ & $|\Delta| < 1$

Where,


$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12} S_{21}|} > 1$$

$$|\Delta| = |S_{11} S_{22} - S_{12} S_{21}| < 1$$

Test for the center of Smith chart

$$\text{If } Z_L = Z_0 \Rightarrow |M_{in}| = |S_{11}|$$

> If $|S_{11}| < 1 \rightarrow |M_{in}| < 1$ for $Z_L = Z_0 \Rightarrow$ Center of Smith chart is stable. Now we can identify if inside or outside the stability circles is stable.

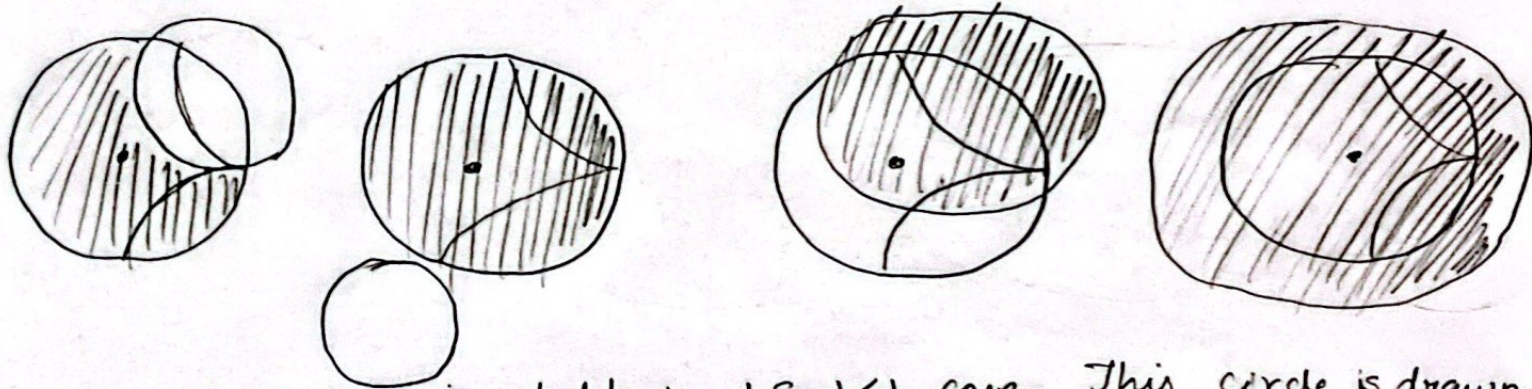

> Shaded region is stable for $|S_{11}| < 1$ case. This circle is drawn at one frequency. Different frequencies have different circles.

> Pick any load in the shaded region and the circuit would be stable.

> Unconditional stability $\rightarrow$ entire Smith chart is stable since it represents all passive impedances.

Amplifier Design.

Unilateral

> Match input and output separately to get $G_{Tmax} = \frac{1}{1-|S_{11}|^2} |S_{21}|^2 \frac{1}{1-|S_{22}|^2}$

$$\Gamma_{in} = S_{11}, \quad \Gamma_{out} = S_{22}$$

$$Z_s = Z_{in}^*, \quad Z_L = Z_{out}^*$$


$$\Gamma_s = S_{11}^*, \quad \Gamma_L = S_{22}^* \rightarrow \text{use this to get } Z_s \text{ \& } Z_L \text{ that give max gain.}$$

> This maximizes G_s \& G_L \& we in fact get gain > 1 from $G_s \times G_L$

> If input \& output are matched does it not imply $S_{11} = 0$ \& $S_{22} = 0$?

$\Rightarrow \Gamma_s \text{ \& } \Gamma_L = 0 \Rightarrow G_{Tmax} = |S_{21}|^2$? No, here S_{11} \& S_{22} are of the device. S_{11}' \& S_{22}' are in fact 0 but these are for the

entire 2 port including the device.

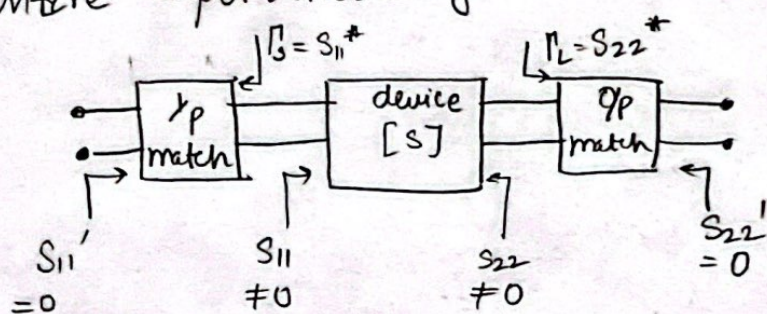

> Unilateral approximation.

Error in transducer gain = $\frac{G_T}{G_{TU}}$ by making the unilateral approximation

This error is bounded by $\frac{1}{(1+U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1-U)^2}$

Where $U = \frac{|S_{21}| |S_{12}| |S_{11}| |S_{22}|}{(1-|S_{11}|^2)(1-|S_{22}|^2)} \rightarrow \text{unilateral figure of merit}$

In general $U \leq 0.1 \Rightarrow \text{make the approximation.}$

Bilateral amplifier design.

Simultaneous conjugate matching.

$$\Rightarrow \Gamma_S^* = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = \Gamma_{in}$$

$$\Gamma_L^* = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S} = \Gamma_{out}$$

$$\Rightarrow \Gamma_{ms} = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$\Gamma_{ml} = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2}$$

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$$

$$B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^*$$

$$C_2 = S_{22} - \Delta S_{11}^*$$

∴ Maximum available gain

$$G_{Tmax} = \frac{1}{1 - |\Gamma_{ms}|^2} |S_{21}|^2 \frac{1}{1 - |\Gamma_{ml}|^2}$$

$$G_{Tmax} = \frac{|S_{21}|}{|S_{12}|} \left(K + \sqrt{K^2 - 1} \right)$$

K is only defined if $|S_{12}| > 0$
since $K \propto \frac{1}{|S_{12}|}$

Simultaneous conjugate match is

only possible if $K > 1 \Rightarrow$ unconditional stability!

Note

$B_1 > 0 \Rightarrow$ use -ve sign

$B_1 < 0 \Rightarrow$ use +ve sign

$B_2 > 0 \Rightarrow$ use -ve sign.

$B_2 < 0 \Rightarrow$ use +ve sign.

When $K=1$ we get max
Stable gain MSG

$$MSG = \frac{|S_{21}|}{|S_{12}|}$$

↳ Cannot go to ∞ if $|S_{12}| = 0$
Since $K \rightarrow \infty$ & G_{Tmax} defn
doesn't make sense.

Constant gain circles.

(35)

- Locus of Γ_s or Γ_L which provides constant gain (G_s or G_L)

Unilateral

$$G_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} \quad \times \quad G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$\Gamma_s = S_{11}^* \quad \& \quad \Gamma_L = S_{22}^* \Rightarrow \text{max gain} \quad G_{s \max} = \frac{1}{1 - |S_{11}|^2} \quad \& \quad G_{L \max} = \frac{1}{1 - |S_{22}|^2}$$

$$\text{Normalized gains: } g_s = \frac{G_s}{G_{s \max}} \quad \& \quad g_L = \frac{G_L}{G_{L \max}}$$

$$g_s = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} (1 - |S_{11}|^2) \quad 0 \leq g_s \leq 1$$

$$g_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} (1 - |S_{22}|^2) \quad 0 \leq g_L \leq 1$$

$g_s, g_L = \text{constant} \Rightarrow$ circles on Γ plane.

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$R_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$R_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

Filters.

- 2 methods:
- Insertion loss method.
 - Image parameter method.

Insertion loss method. $P_{LR} = \frac{1}{|S_{12}|^2}$ if load & source are matched.

$$P_{LR} = \overset{10 \log P_{LR}}{\text{Insertion loss}} = \frac{\text{Power available from source}}{\text{Power delivered to load}} = \frac{P_{avs}}{P_{load}} = \frac{1}{1 - |\Gamma_{load}|^2}$$

In general,

$$P_{LR} = 1 + \frac{M(\omega^2)}{N(\omega^2)} \quad \text{where } M \& N \text{ are polynomials.}$$

if matched $IL = 10 \log P_{LR} = -20 \log |S_{12}|$

Maximally flat aka Butterworth aka Binomial. response.

$$P_{LR} = 1 + K^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$

$\omega_c \rightarrow$ cut off freq
 $N \rightarrow$ number of lumped elements aka order.

→ Flattest possible passband, slow roll off.

Equiripple aka Chebyshev response.

$$P_{LR} = 1 + K^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)$$

$T_N(x)$ is the Chebyshev polynomial of the first kind of order N .

→ Fast roll off & ripple in passband.

Elliptic response.


> look up table

> Fastest roll off with ripple in pass & stop band.


Steps in Insertion Loss method.

- Based on specs, design a prototype.
- Using scaling & conversion rules, obtain the desired filter.
- Implement filter using lumped elements or transmission lines.

Lowpass prototypes.

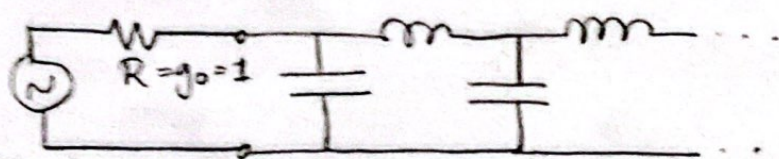

Reflects as a short as $f \uparrow$

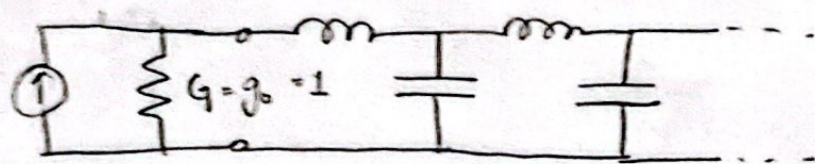

Reflects as an open as $f \uparrow$

$\Rightarrow$ phase response is different

$$g_0 = \begin{cases} \text{generator resistance for } \Pi \\ \text{generator conductance for } T \end{cases}$$

$$g_k \quad k=1, \dots, N = \begin{cases} \text{inductance for series element} \\ \text{capacitance for shunt element} \end{cases}$$

$$g_{N+1} = \begin{cases} \text{load resistance if } g_N \text{ is shunt cap.} \\ \text{load conductance if } g_N \text{ is series ind.} \end{cases}$$

> For a type of filter g values are got from a Table & design proceeds.

> This is designed for $\omega_c = 1$ $\times g_0 = g_{N+1} = 1$
 $\underbrace{\hspace{10em}}_{\text{not always 1}}$

Filter Transformations.

→ Impedance scaling.

$$L' = Z_0 L$$

$$R_s' = Z_0$$

→ where Z_0 is the source resistance.

$$C' = \frac{C}{Z_0}$$

$$R_L' = Z_0 R_L$$

→ Frequency scaling.

Scale the frequency response by $\frac{1}{\omega_c}$ → replace $\omega \rightarrow \frac{\omega}{\omega_c}$

$$\therefore L_k' = \frac{L_k}{\omega_c}, \quad C_k' = \frac{C_k}{\omega_c}.$$

⇒ Combining the 2 scaling laws:

$$L_k' = \frac{Z_0 L_k}{\omega_c}$$

$$C_k' = \frac{C_k}{Z_0 \omega_c}.$$

→ Low pass to high pass transformation.

$$\omega \rightarrow -\frac{\omega_c}{\omega}$$

$$C_k' = \frac{1}{Z_0 \omega_c L_k}$$

inductor → cap

$$L_k' = \frac{Z_0}{\omega_c C_k}.$$

cap → ind.

Band Pass/Stop transformation.


$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0} \rightarrow \text{Fractional Bandwidth.}, \omega_0 = \sqrt{\omega_1 \omega_2}.$$

$$\omega \rightarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{\Delta} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

$$\omega_0 = \text{center frequency} = \sqrt{\omega_1 \omega_2}$$


use $\left| \frac{\omega}{\omega_0} \right| - 1$ to find N on the table

Band pass.

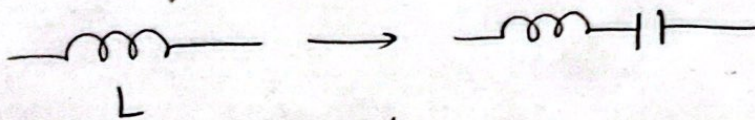

$$L_k' = \frac{L_k Z_0}{\Delta \omega_0} \quad \xrightarrow{g_k}$$

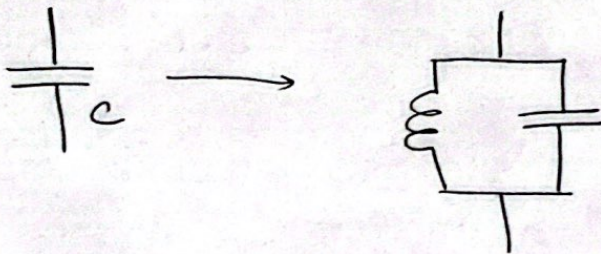
$$C_k' = \frac{\Delta}{\omega_0 L_k Z_0} \quad \xrightarrow{g_k}$$



$$L_k' = \frac{\Delta Z_0}{\omega_0 C_k} \rightarrow g_k$$


$$C_k' = \frac{C_k \rightarrow g_k}{\Delta \omega_0 Z_0}$$

Band stop.

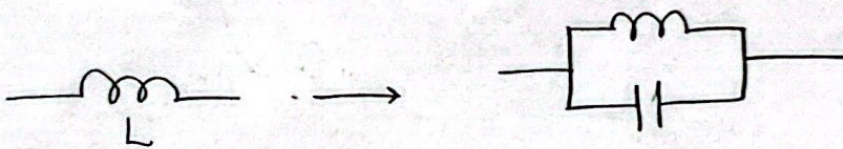

$$L_k' = \frac{\Delta L_k Z_0}{\omega_0}$$
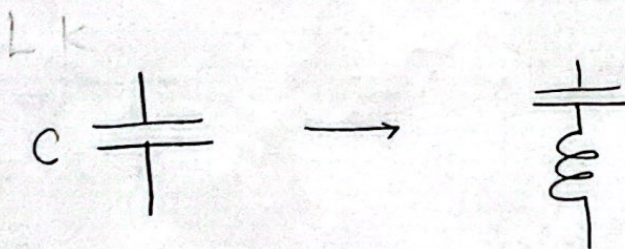
$$C_k' = \frac{1}{\omega_0 \Delta L_k Z_0}$$






$$L_k' = \frac{Z_0}{\omega_0 \Delta C_k}$$

$$C_k' = \frac{\Delta C_k}{\omega_0 Z_0}$$

Filter Implementation.

→ Implementing lumped elements as T Lines.

Richards Transformation.

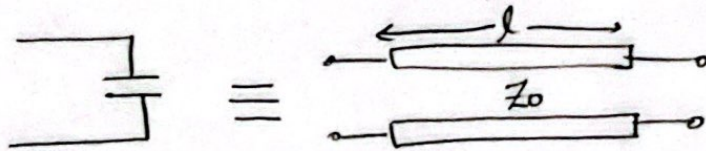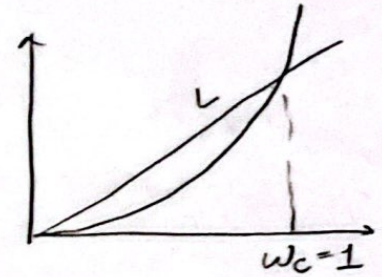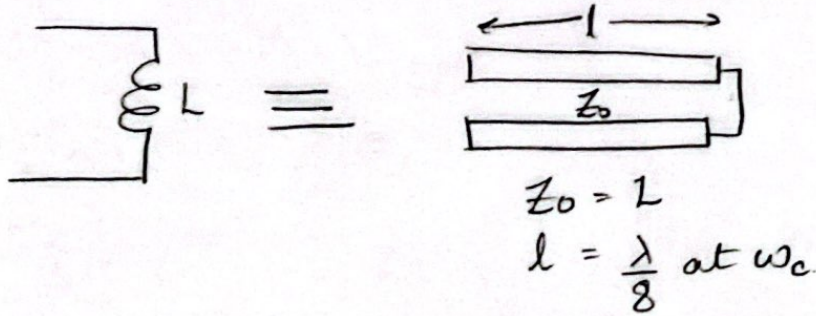

$$Y_0 = C \Rightarrow Z_0 = \frac{1}{C}$$


$$l = \frac{\lambda}{8} \text{ at } \omega_c$$

- Frequency response becomes periodic → problem!!
- Impedance Scaling must be done by multiplying Z_0 with desired filter impedance.
- Problem: Series stubs cannot be fabricated in planar process.

Kuroda's Identity.

- To separate stubs.
- To transform Series stubs to shunt stubs
- To get realisable characteristic impedances.
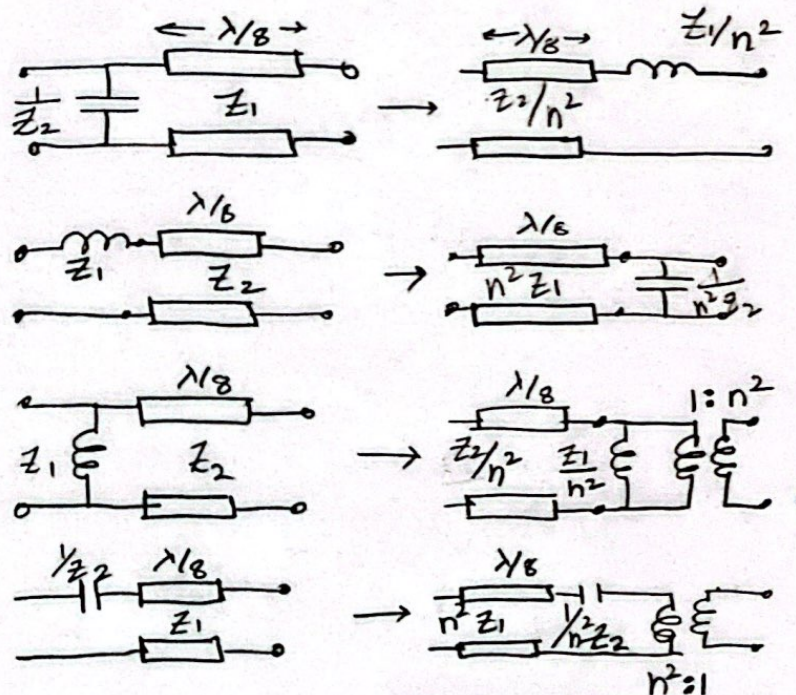
$$\rightarrow n^2 = 1 + \frac{Z_2}{Z_1}$$




Stepped Impedance Low Pass Filters.

- Series inductor → high impedance line ($\beta l < \lambda/4$)
- Shunt capacitor → low impedance line ($\beta l < \lambda/4$)

$$\rightarrow L = \frac{Z_h l}{U_p} = \frac{Z_h \beta l}{\omega}$$

$$C = \frac{\beta l}{\omega Z_l}$$

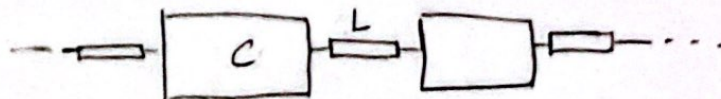

→ $\frac{Z_h}{Z_l}$ should be as large as possible.


$$\rightarrow \beta l = \frac{Z_0 k}{Z_h} \text{ for series inductor.}$$

$$\beta l = \frac{C_k Z_l}{Z_0} \text{ for shunt capacitor.}$$

Inverters.

Transform load impedance to its inverse.

→ $\lambda/4$ line.

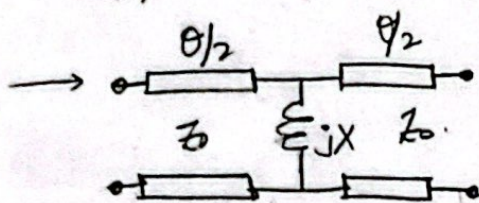


$$K = Z_0 \tan(\theta/2)$$

$$X = \frac{K}{1 - |K/Z_0|^2}$$

$$\theta = -\tan^{-1} \frac{2X}{Z_0}$$

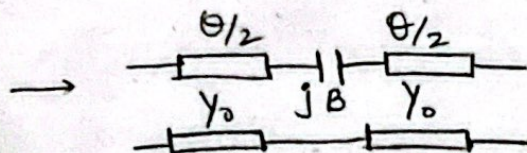θ_0 is -ve $\Rightarrow$ it can be absorbed into existing lines.



$$J = Y_0 \tan(\theta/2)$$

$$B = \frac{J}{1 - (J/Y_0)^2}$$

$$\theta = -\tan^{-1} \frac{2B}{Y_0}$$

→ Band pass & Band stop filters using $\frac{\lambda}{4}$ resonators.


> An open circuited $\lambda/4$ Tline with characteristic impedance Z_{0n} acts like a series resonant circuit.

$$\rightarrow \omega_0 L_n = \frac{\pi}{4} Z_{0n} \quad \text{where } \omega_0 = \frac{1}{\sqrt{L_n C_n}}$$


> Short circuit $\lambda/4 \rightarrow$ parallel resonant circuit.

$$\rightarrow \omega_0 C_n = \frac{\pi}{4} \cdot \frac{1}{Z_{0n}} \quad \text{where } \omega_0 = \frac{1}{\sqrt{L_n C_n}}$$

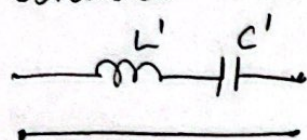→ Convert series resonant circuit $\rightarrow$ parallel using inverters.





$\equiv$

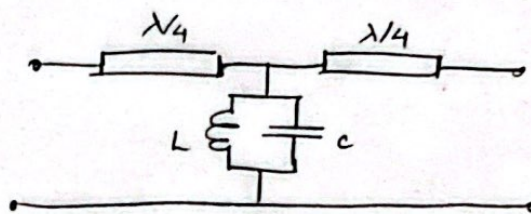

K inverter

$$L = \frac{Z_0^2}{\omega_0^2 L'}$$

$$C = \frac{1}{\omega_0^2 C' Z_0^2}$$

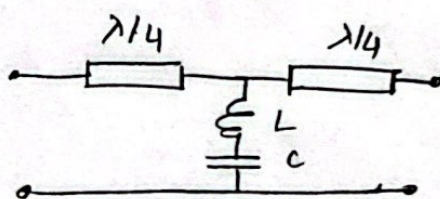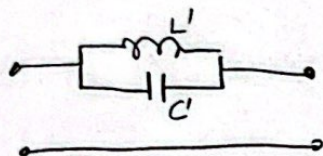


J inverter

Steps.

- 1) Choose filter type (# of sections, g values)
- 2) Use filter transformations
- 3) Determine L_k s & C_k s for resonators.
- 4) Transform series resonators to shunt resonators as shown above.
- 5) Implement all shunts with $\lambda/4$ s-c Tlines (or open circuit in case of band stop - refer to top of this page).

Image Impedance of 2 port networks.

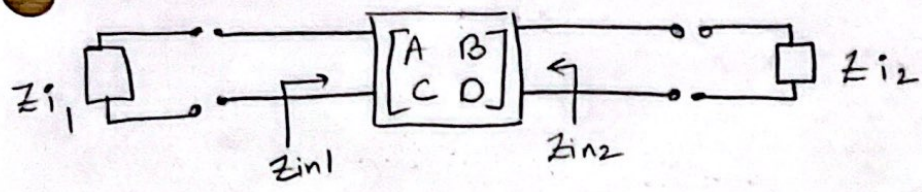

→ If connecting Z_{i1} & Z_{i2} ensures $Z_{in1} = Z_{i1}$ & $Z_{in2} = Z_{i2}$ we call Z_{i1} & Z_{i2} image impedances of the 2 port.


$$\rightarrow Z_{i1} = \sqrt{\frac{AB}{CD}} \quad Z_{i2} = \sqrt{\frac{BD}{AC}}$$

→ Symmetric network $\Rightarrow Z_{i1} = Z_{i2}$ since $A=D$


$$\frac{V_2}{V_1} = \sqrt{\frac{D}{A}} (\sqrt{AD} - \sqrt{BC})$$

$$\frac{I_2}{I_1} = \sqrt{\frac{A}{D}} (\sqrt{AD} - \sqrt{BC})$$
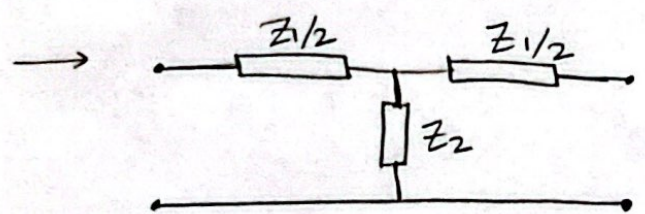
$$e^{-\gamma} = \sqrt{AD} - \sqrt{BC} \text{ where } \gamma = \alpha + j\beta$$



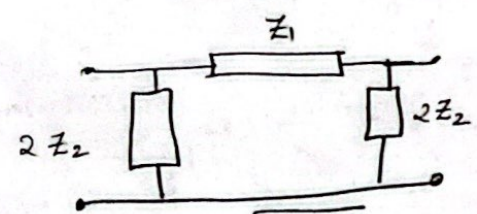
$$Z_i = \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4Z_2}}$$



$$Z_i = \frac{\sqrt{Z_1 Z_2}}{\sqrt{1 + \frac{Z_1}{4Z_2}}}$$

$$e^{\gamma} = 1 + \frac{Z_1}{2Z_2} + \sqrt{\frac{Z_1}{Z_2} + \frac{Z_1^2}{4Z_2^2}}$$

Coupled Tline

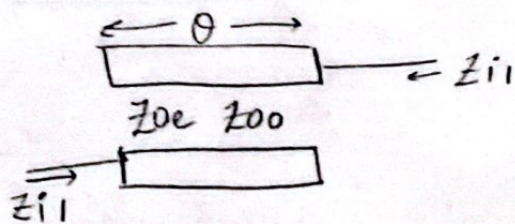


$$Z_i = \frac{1}{2} \sqrt{(Z_{0e} - Z_{0o})^2 \operatorname{cosec}^2 \theta - (Z_{0e} + Z_{0o}) \cot^2 \theta}$$

when $\theta = \frac{\pi}{4}$

$$Z_i = \frac{1}{2} (Z_{0e} - Z_{0o})$$

$$\cos \theta = \frac{Z_{0e} + Z_{0o}}{Z_{0e} - Z_{0o}} \cos \theta$$

} Band pass response.

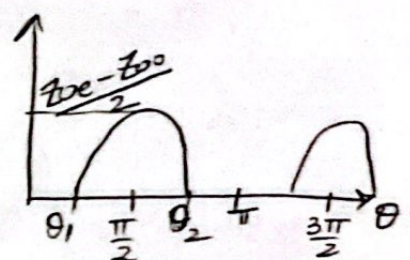

→ Cascading them gives desired response.

Recipe.

$$\Delta = \frac{\omega_2 - \omega_1}{\omega_0}$$

$$\frac{\omega}{\omega_c} \leftarrow \frac{\omega_0}{\omega_2 - \omega_1} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)$$

$$\left| \frac{\omega}{\omega_c} \right| - 1 \text{ gives } N$$

$$J_1 Z_0 = \sqrt{\frac{\pi \Delta}{2 g_1}}$$

$$J_n Z_0 = \frac{\pi \Delta}{2 \sqrt{g_{n-1} g_n}}$$

$$J_{n+1} Z_0 = \sqrt{\frac{\pi \Delta}{2 g_n g_{n+1}}}$$

$$Z_{0e} = Z_0 [1 + J Z_0 + (J Z_0)^2]$$

$$Z_{0o} = Z_0 [1 - J Z_0 + (J Z_0)^2]$$

$$\theta = \frac{\pi}{2}$$

Mixers

→ Conversion loss in dB = $10 \log \frac{\text{IF output power}}{\text{RF input power}}$

Typical diode mixers → Loss = 6dB.


→ In case of passive mixers, the noise figure is atleast equal to the loss.

→ LO-RF isolation in dB = $10 \log \frac{\text{LO power (leak) at RF port}}{\text{LO input power}}$


→ RF-IF isolation in dB = $10 \log \frac{\text{RF power at IF port}}{\text{Input RF power}}$

→ LO-IF isolation in dB = $10 \log \frac{\text{LO power at IF port}}{\text{LO input power}}$



Single ended diode mixer

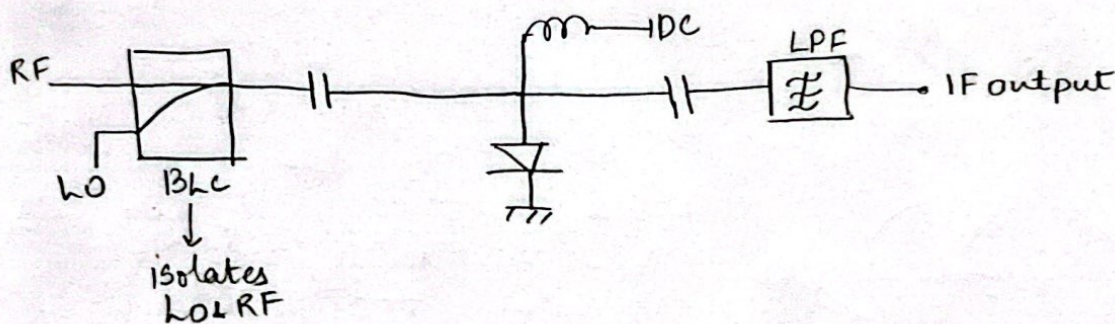

Single ended FET mixer

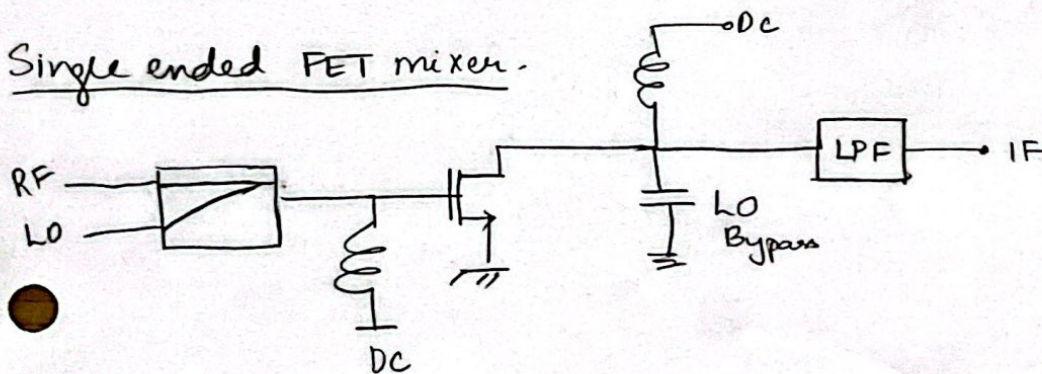

Switching Type Mixers

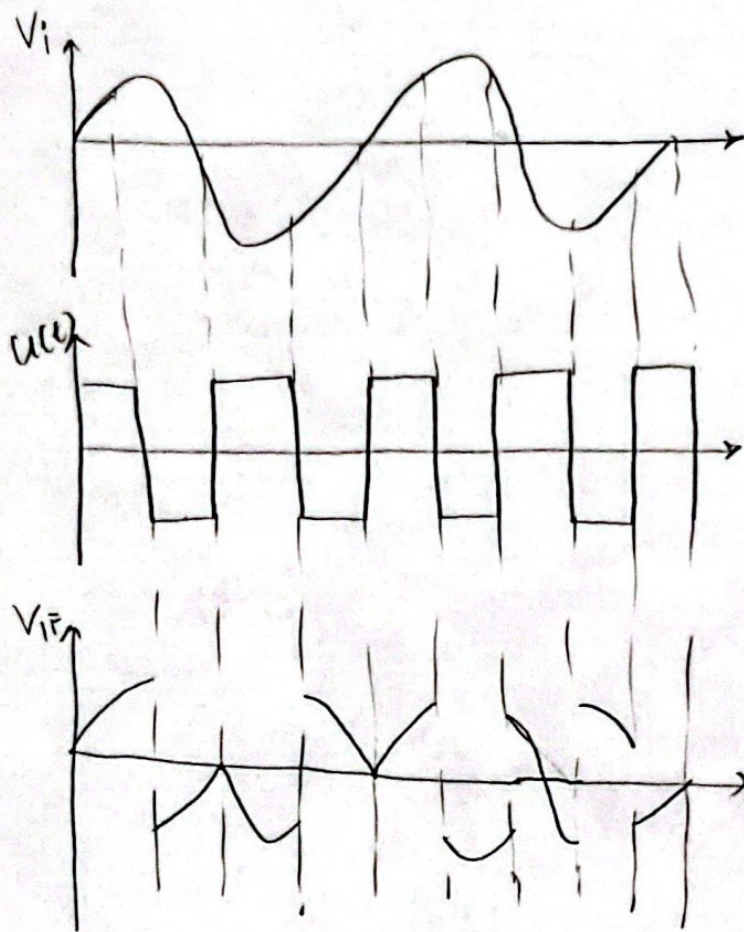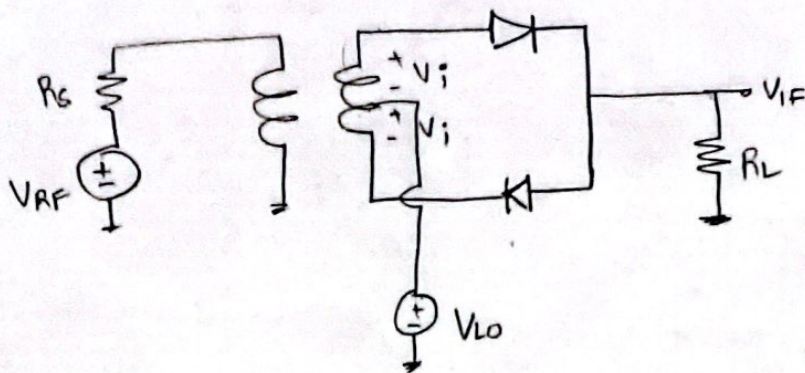

$$V_{LO} > 0 \Rightarrow u(t) = 1$$

$$V_{LO} < 0 \Rightarrow u(t) = -1$$


$$V_i = V_i \sin \omega_i t$$

$$u(t) = \frac{4}{\pi} [\sin \omega_{LO} t + \sin 3\omega_{LO} t + \dots]$$

$$V_{IF} = V_{LO} + u(t) V_i$$

→ LO leaks to IF port

→ To prevent this use a balanced mixer.

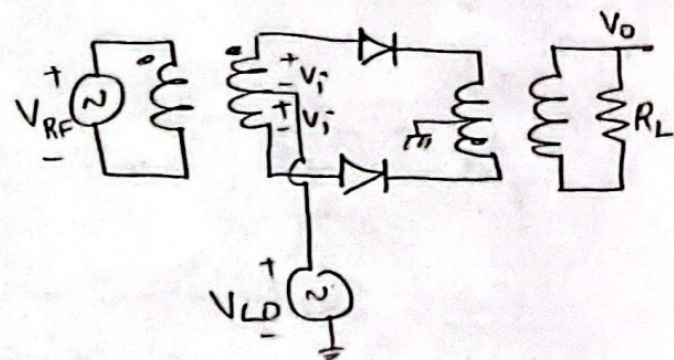


$$V_{LO} > 0 \Rightarrow \text{Both diodes are ON} \Rightarrow V_O = V_i$$

$$V_{LO} < 0 \Rightarrow \text{Both are OFF} \Rightarrow V_O = 0$$

⇒ Sampling mixer!

Balanced mixer at microwave.

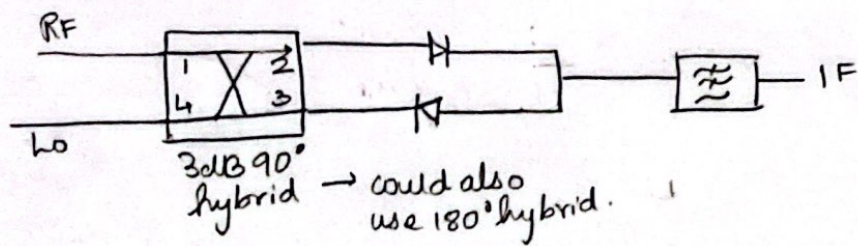

Double Balanced Mixer.


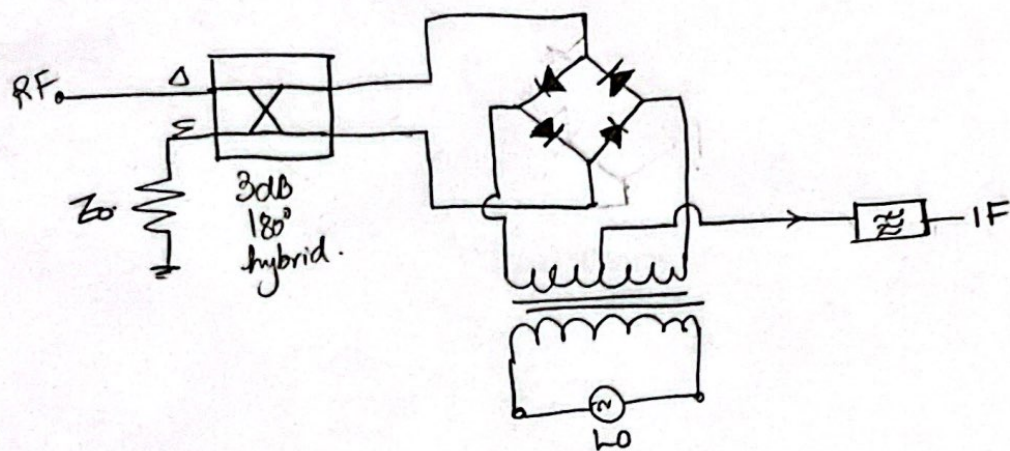



Image Reject Mixers

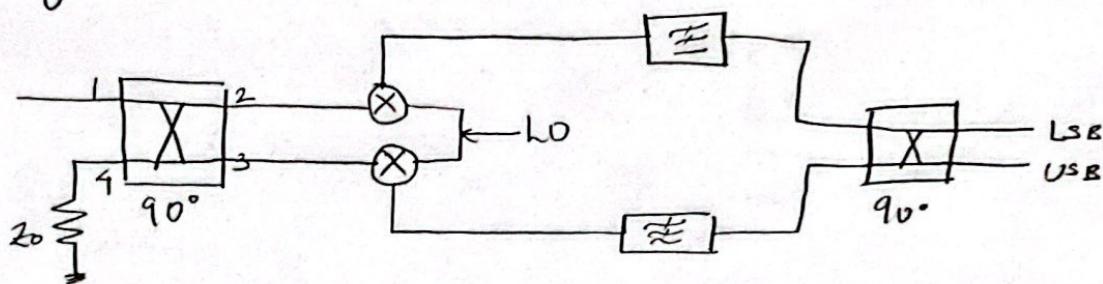


Receiver Basics.

Image frequency → Downconverter.

$f_{RF} > f_{LO}$

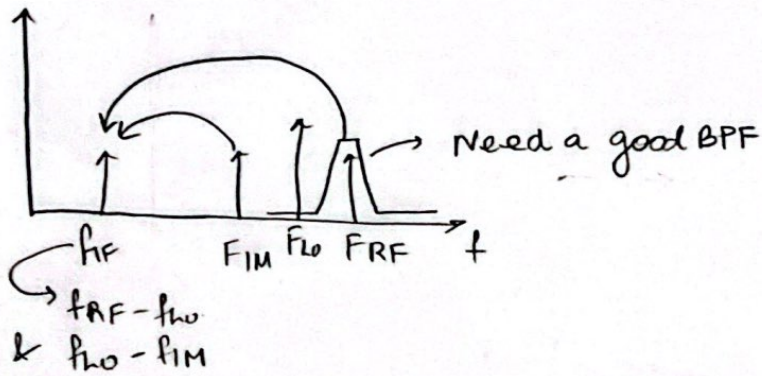


$f_{RF} < f_{LO}$

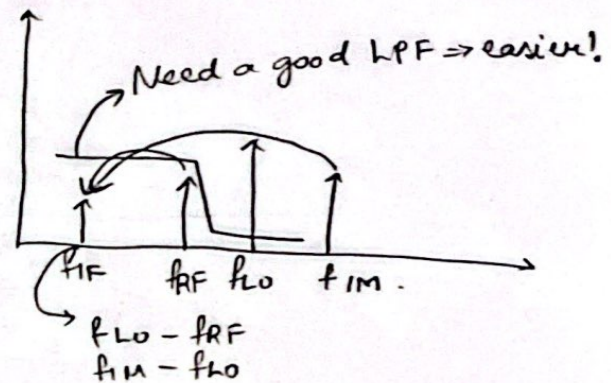


Upconverter

$f_{RF} > f_{LO}$

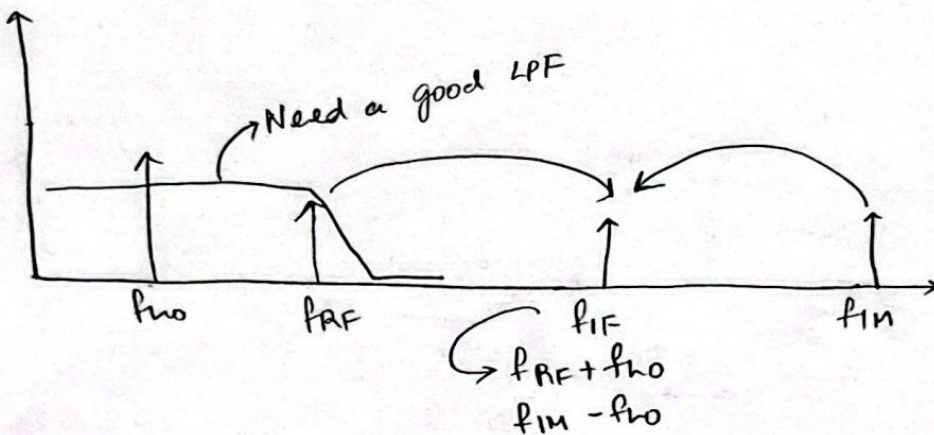




$f_{RF} < f_{LO}$

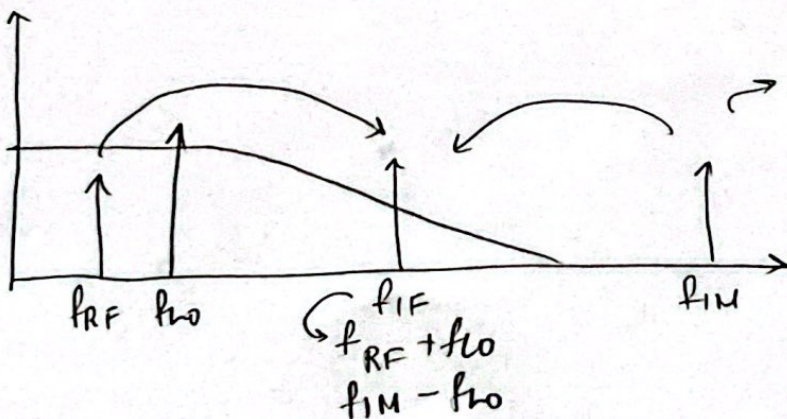

Since f_{LO} is higher than earlier, f_{IM} must be much higher to fall on f_{IF} therefore a shallow roll off LFP does the job.

→ In both up & down converters, in case of $f_{RF} < f_{LO}$ notice that as $f_{LO} \uparrow$, $f_{IM} \uparrow \uparrow$, therefore LPF design specs become easier. High $f_{LO} \Rightarrow$ good for image rejection.

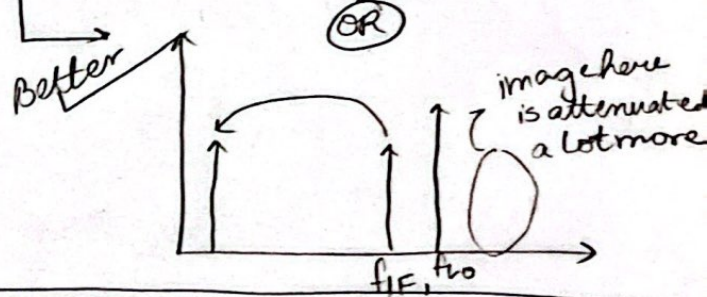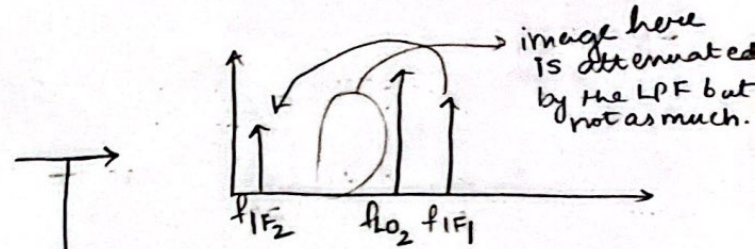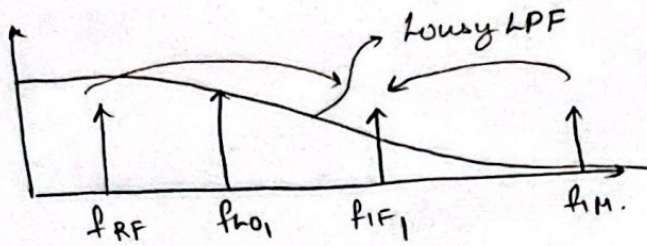→ Dual conversion mixers. → First up convert → LPF for images then downconvert.



Receiver Sensitivity

$$P_{in, min} (dBm) = -174 + 10 \log(BW_{channel}) + NF (dB) + SNR_{out, min} (dB)$$

↓
min SNR at out for a specified BER or modulation


Microwave Resonators

$$Q = \omega \cdot \frac{\text{average energy stored}}{\text{energy loss/second}}$$

$$Q = \omega \cdot \frac{W_m + W_e}{P_{\text{loss}}} = \omega \frac{2W_m}{P_{\text{loss}}} \quad \text{at resonance}$$

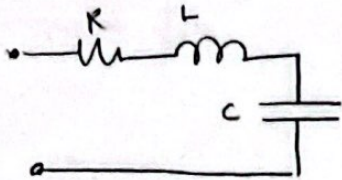a) Input impedance of series resonator

$$Q = \frac{1}{\omega_0 R C} = \frac{\omega_0 L}{R}$$




$$Z_{\text{in}} = R + 2j \frac{RQ}{\omega_0} \Delta\omega$$

$$Z_{\text{in}} = R \left(1 + 2j \frac{Q \Delta\omega}{\omega_0} \right)$$

$$Z_{\text{in}} = \frac{\omega_0 L}{Q} + j 2L(\omega - \omega_0)$$

$\Rightarrow R = \frac{\omega_0 L}{Q}$. Therefore a lossless resonator can be made lossy in analysis by $\omega_0 \rightarrow \omega_0 \left(1 + \frac{j}{2Q} \right)$

$$BW = \frac{\omega_0}{Q}$$

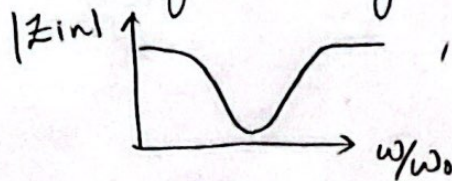


b) Input impedance of parallel resonator

$$Z_{\text{in}} = \left(\frac{1}{R} + j \frac{\Delta\omega}{\omega_0^2 L} + j \Delta\omega C \right)^{-1} = \frac{R}{1 + j \frac{2Q \Delta\omega}{\omega_0}}$$

Again replace $\omega_0 \rightarrow \omega_0 \left(1 + \frac{j}{2Q} \right)$ to make it lossy.

$$BW = \frac{\omega_0}{Q}$$

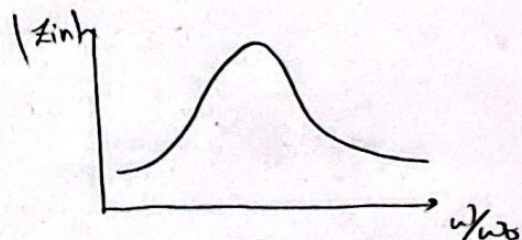

Loaded Q_L


Series resonant circuit $\Rightarrow Q_L = \frac{\omega_0 L}{R + R_L}$

Parallel resonant circuit $\Rightarrow Q_L = \frac{RR_L / (R + R_L)}{\omega_0 L}$

$$\boxed{\frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q}} \quad \begin{array}{l} \text{loaded } Q \text{ with lossy resonator.} \\ \text{unloaded } Q \text{ with lossy resonator.} \\ \text{loaded } Q \text{ with lossless resonator.} \end{array}$$

Transmission line resonator
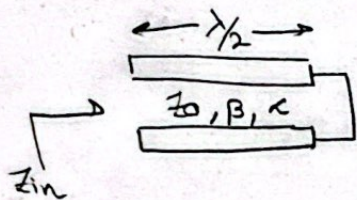
> Short circuit $\lambda/2$ line acts as a series resonant circuit.



lossless $\Rightarrow Z_{in} = j Z_0 \tan \beta l$

lossy $\Rightarrow Z_{in} = \frac{Z_0 \tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$

Near resonance, $\omega = \omega_0 + \Delta\omega$

$$\beta l = \frac{\omega l}{v_p} = \frac{\omega_0 l}{v_p} + \frac{\Delta\omega l}{v_p}$$

$$\text{at } \omega_0: l = \frac{\lambda}{2} = \frac{v_p}{2f_0} = \frac{\pi v_p}{\omega_0} \Rightarrow \beta l = \pi + \frac{\Delta\omega \pi}{\omega_0}$$

$$\tan \beta l \approx \frac{\Delta\omega \pi}{\omega_0} \quad \text{if } \alpha \text{ is small } \tanh \alpha l \approx \alpha l$$

$$\Rightarrow Z_{in} = Z_0 \left(\alpha l + j \frac{\Delta\omega \pi}{\omega_0} \right)$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\text{Let } R = Z_0 \alpha l$$


$$L = \frac{Z_0 \pi}{2 \omega_0}$$

$$C = \frac{2}{Z_0 \pi \omega_0}$$

$$\theta = \frac{\pi}{2 \alpha l} = \boxed{\frac{\beta}{2 \alpha}} \rightarrow \text{conductor loss} + \text{dielectric loss.}$$

→ Short circuit $\frac{\lambda}{4}$ line behaves like a parallel resonant circuit.
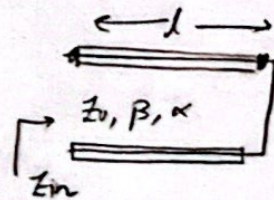
$$Z_{in} = \frac{1}{\frac{\alpha l}{Z_0} + j \frac{\pi}{2} \frac{\Delta \omega}{\omega_0 Z_0}}$$




$$\Rightarrow R = \frac{Z_0}{\alpha l}, \quad C = \frac{\pi}{4 \omega_0 Z_0}, \quad \theta = \omega_0 RC \Rightarrow \boxed{\theta = \frac{\beta}{2 \alpha}}$$

→ open circuit $\frac{\lambda}{2}$ line $\equiv$ Parallel resonant circuit

$$R = \frac{Z_0}{\alpha l}; \quad C = \frac{\pi}{2 \omega_0 Z_0}; \quad L = \frac{1}{\omega_0^2 C}; \quad \theta = \frac{\beta}{2 \alpha}$$


→

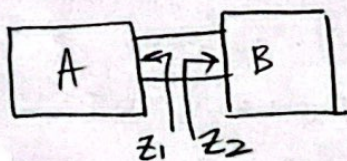

If AB constitute a resonant circuit,
at resonance $Z_1 = Z_2^*$

Excitation of Resonators

Critical Coupling.

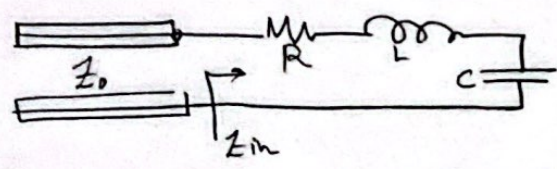

At resonance $Z_{in} = R \Rightarrow$ great!
 $\Rightarrow$ Critical coupling.


Coupling coefficient $g = \frac{\text{loss } R + \text{load loss}}{\text{no loss} + \text{load loss. (} \beta \text{ external)}}$

Series resonance $\Rightarrow g = \frac{Z_0}{R}$


parallel resonance $\Rightarrow g = \frac{R}{Z_0}$

$g = 1 \Rightarrow$ The resonator is critically coupled.

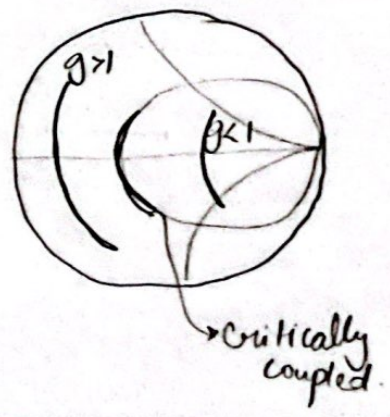
$g < 1 \Rightarrow$ undercoupled } Bad.
 $g > 1 \Rightarrow$ over coupled }



Gap Coupling.

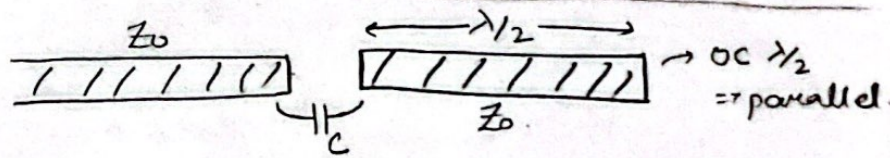

$$\tan \beta l = -Z_0 \omega c$$

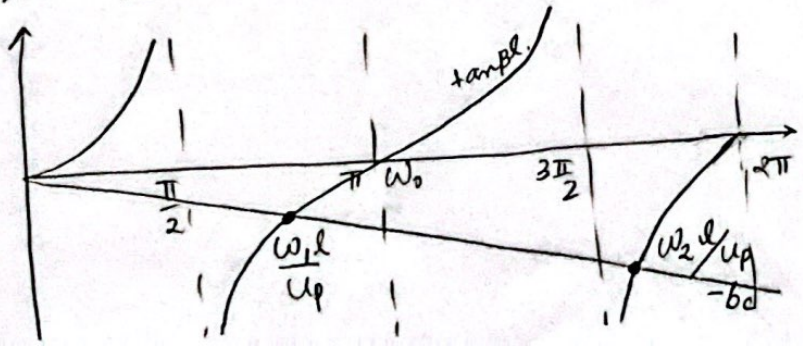


Gap coupling reduces the resonant frequency from $\omega_0 \rightarrow \omega_1$. If $bc \ll 1 \Rightarrow \omega_1$ is close to ω_0 .

At resonance $R = \frac{Z_0 \pi}{2B b_c^2} \Rightarrow \boxed{b_c = \sqrt{\frac{\pi}{2B}}}$ For critical coupling

$$\boxed{g = \frac{2B b_c^2}{\pi}}$$

→ Approximate theory of multisection quarter wave transformers for wideband impedance matching.

Theory of small reflections.

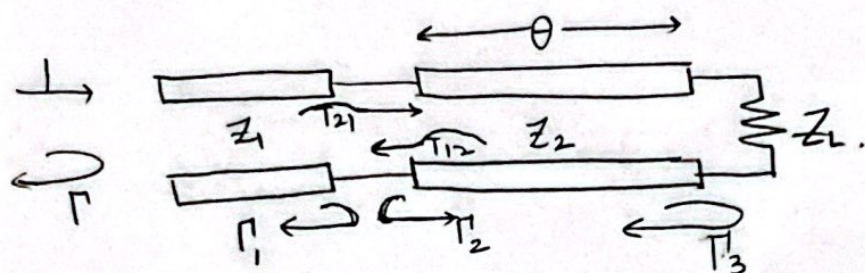

$$\boxed{\Gamma \approx \Gamma_1 + \Gamma_3 e^{-2j\theta}}$$


Book has the full proof.

→ This idea can be extended to multisection $\frac{\lambda}{4}$ line matching & tapered wideband matching.

Bode-Fano Criteria.

Parallel RC network as load.

$$\int_0^\infty \ln \frac{1}{|\Gamma(\omega)|} d\omega \leq \frac{\pi}{RC}.$$

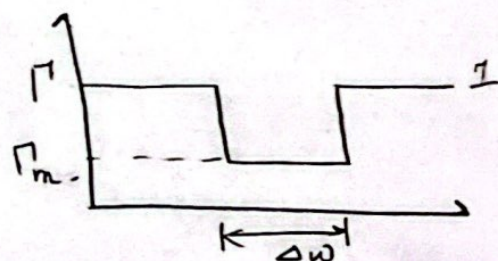

$\Gamma(\omega) = 0$ at some point $\Rightarrow$ the width of the match must be 0.
 $\Rightarrow$ 0 BW.

→ Similar formula exist for series RC & RL loads.